

# Prayas JEE (2025)


## Physics

### Capacitor

**DPP: 5**

**Q1** Find out the following if *A* is connected with *C* and *B* is connected with *D*.

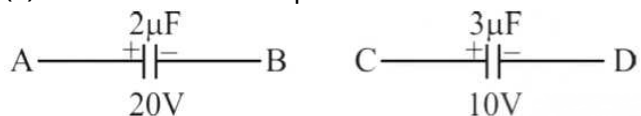- (i) How much charge flows in the circuit.
- (ii) How much heat is produced in the circuit.




- Q2** In a charged capacitor, the energy resides
- (A) The positive charges
  - (B) Both the positive and negatives charges
  - (C) In the field between the plates
  - (D) Around the edge of the capacitor plates

- Q3** 64 drops each having the capacity *C* and potential *V* are combined to form a big drop. If the charge on the small drop is *q*, then the charge on the big drop will be
- (A) 2*q*
  - (B) 4*q*
  - (C) 16*q*
  - (D) 64*q*


- Q4** Force of attraction between the plates of parallel plate capacitor is
- (A)  $\frac{q^2}{2\epsilon_0 AK}$
  - (B)  $\frac{q^2}{\epsilon_0 AK}$
  - (C)  $\frac{q}{2\epsilon_0 A}$
  - (D)  $\frac{q^2}{2\epsilon_0 A^2 K}$

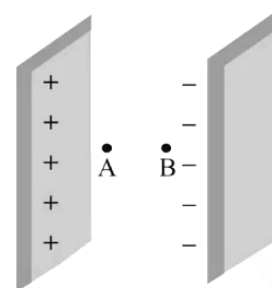- Q5** Two protons *A* and *B* are placed in space between plates of a parallel capacitor charged upto *V* volts. Forces on protons are *F<sub>A</sub>* and *F<sub>B</sub>*, then



- (A)  $F_A > F_B$
- (B)  $F_A < F_B$
- (C)  $F_A = F_B$
- (D) Nothing can be said

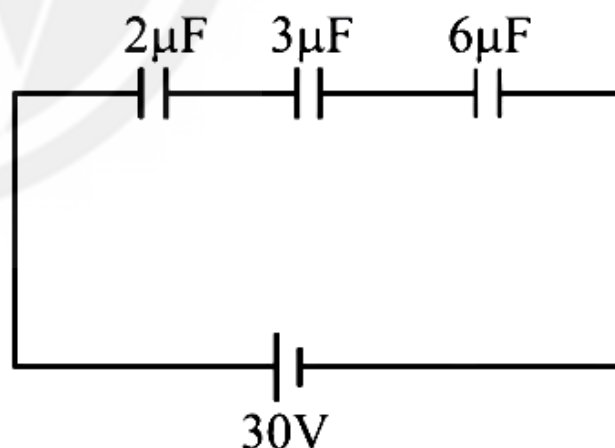- Q6** Three initially uncharged capacitors are connected in series as shown in circuit with a battery of emf 30 V. Find out following
- (i) Charge flow through the battery
  - (ii) Potential energy in 3 µF capacitor
  - (iii)  $U_{total}$  in capacitors




- Q7** Two dielectric slabs of constant *k<sub>1</sub>* and *k<sub>2</sub>* have been filled in between the plates of a capacitor as shown below. What will be the capacitance of the capacitor:



[Android App](#)


[iOS App](#)

[PW Website](#)

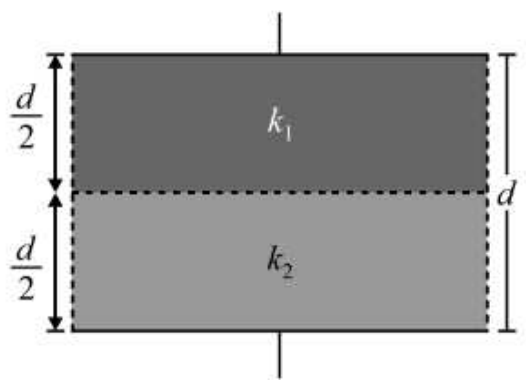

- (A)  $\frac{2\epsilon_0 A}{d} (k_1 + k_2)$
- (B)  $\frac{2\epsilon_0 A}{d} \left( \frac{k_1 + k_2}{k_1 \times k_2} \right)$
- (C)  $\frac{4\epsilon_0 A}{d} \left( \frac{k_1 \times k_2}{k_1 + k_2} \right)$
- (D)  $\frac{2\epsilon_0 A}{d} \left( \frac{k_1 \times k_2}{k_1 + k_2} \right)$

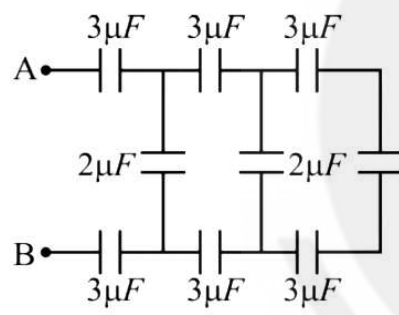**Q8** The resultant capacitance between A and B in the following figure is equal to



- (A)  $1 \mu F$
- (B)  $3 \mu F$
- (C)  $2 \mu F$
- (D)  $1.5 \mu F$

**Q9** A parallel plate capacitor has plates of area  $4 \text{ m}^2$  separated by distance of  $0.5 \text{ mm}$ . The capacitor is connected across a cell of emf  $100 \text{ V}$ .

- (a) Find the capacitance, charge and energy stored in the capacitor.
- (b) A dielectric slab of thickness  $0.5 \text{ mm}$  is inserted inside this capacitor after it has been disconnected from the cell. Find the answer to part (a) if  $k = 3$ .

**Q10** If a dielectric slab of thickness  $t$  and area  $A$  is inserted in between the plates of a parallel

plates capacitor of plate area  $A$  and distance between the plates  $d (d > t)$  then find out capacitance of system. What do you predict about the dependence of capacitance on location of slab?



[Android App](#) | [iOS App](#) | [PW Website](#)

# Answer Key

Q1 (i) 12 uC  
(ii) 60 uJ

Q2 C

Q3 D

Q4 A

Q5 C

Q6 (i)  $30 \mu\text{C}$  (ii)  $150 \mu\text{J}$  (iii)  $450 \mu\text{J}$

Q7 D

Q8 A

Q9 (a)  $C = 7.08 \times 10^{-8} \text{ F}$ ,  $Q = 7.08 \times 10^{-6} \text{ C}$ ,  $U = 3.54 \times 10^{-4} \text{ J}$

(b)  $C = 2.124 \times 10^{-7} \text{ F}$ ,  $Q = 7.08 \times 10^{-6} \text{ C}$ ,  $U = 118 \times 10^{-6} \text{ J}$

Q10 
$$\frac{\epsilon_0 A}{d - t \left(1 - \frac{1}{k}\right)}$$



[Android App](#)

| [iOS App](#)

| [PW Website](#)

ATDB.uno