

PRAYAS

JEE 2025

ATDB.uno

Lecture - 3

Physics

Capacitor

By- Saleem Ahmed Sir





Topics *to be covered*

1

Ceq, Series-parallel

2

Slab inserted b/w Cap. band qus.


3

4

ATDB.uno



ATDB.uno

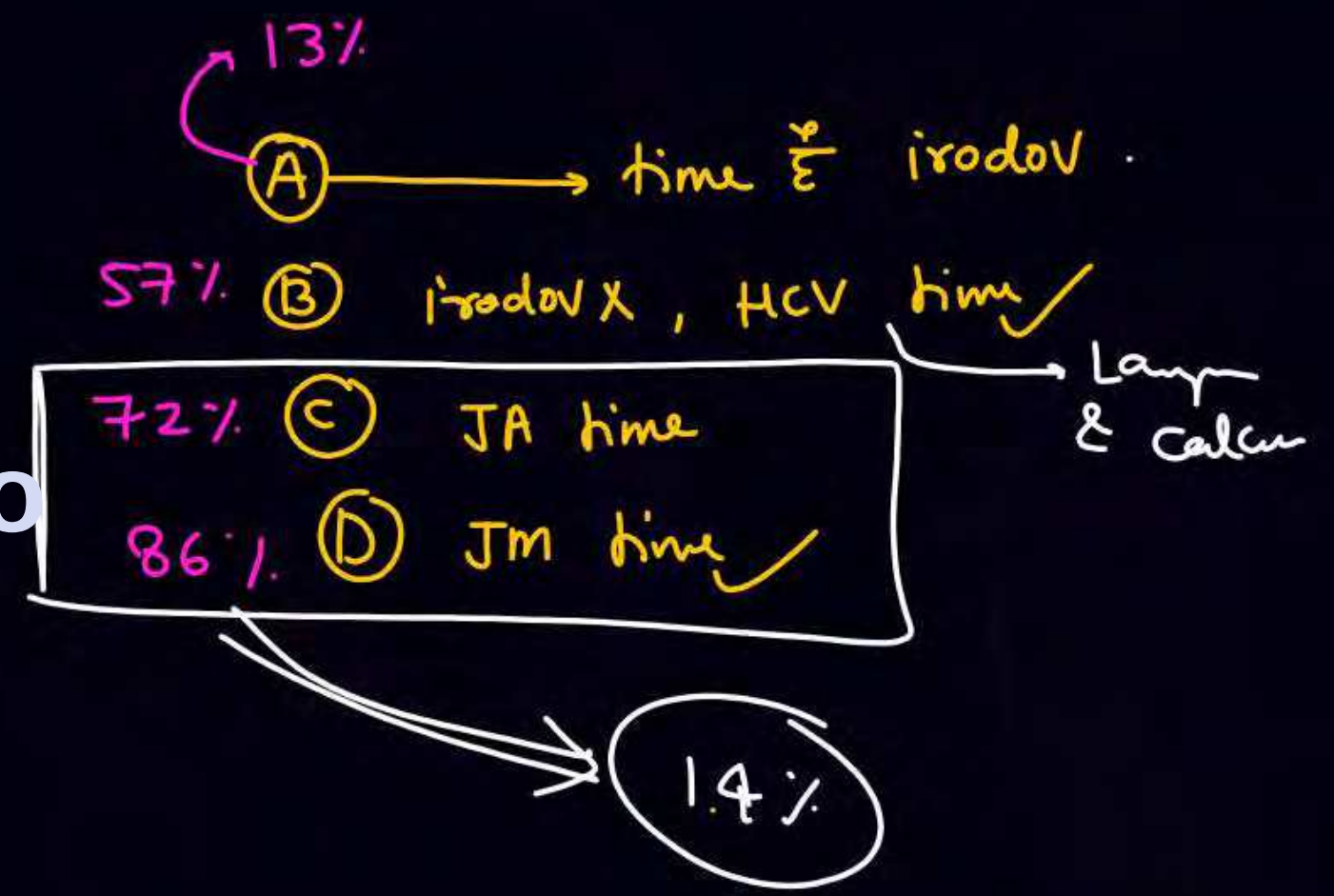


Resistance $\Rightarrow$ series $R_{eq} = R_1 + R_2$
parallel $R_{eq} = ?$
 $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$

Capacitor parallel $\Rightarrow C_{eq} = C_1 + C_2 + C_3 + \dots$

Capacitor Series $\Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$

1

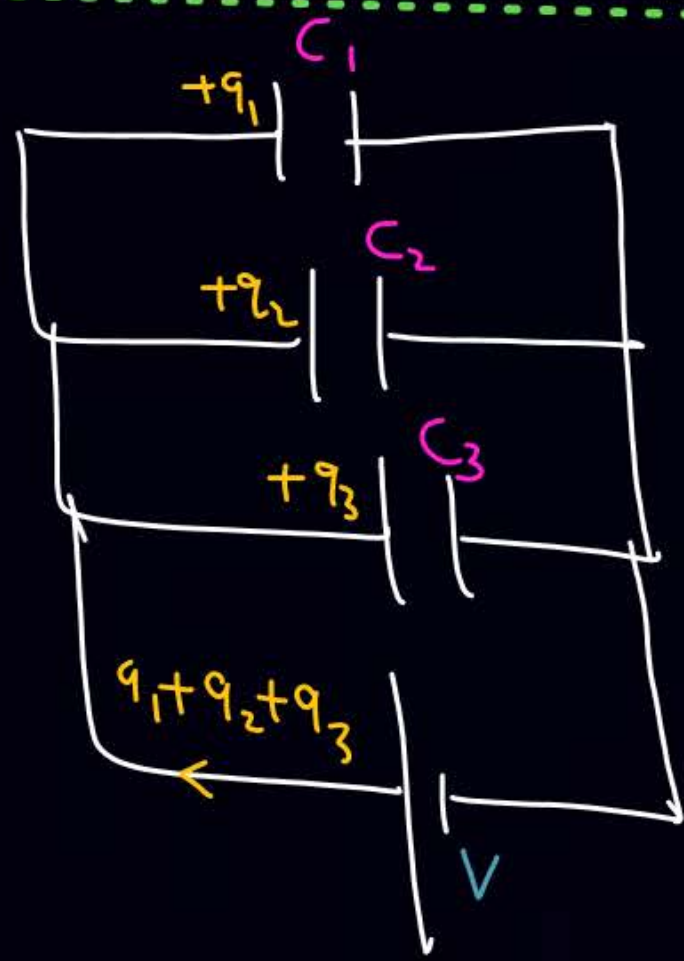


ATDB.uno



$$q_1 + q_2 + q_3 = C_1 V + C_2 V + C_3 V = q_{net}$$



$C_{eq} = C_1 + C_2 + C_3 + \dots$

$$= C_{eq} \cdot V$$

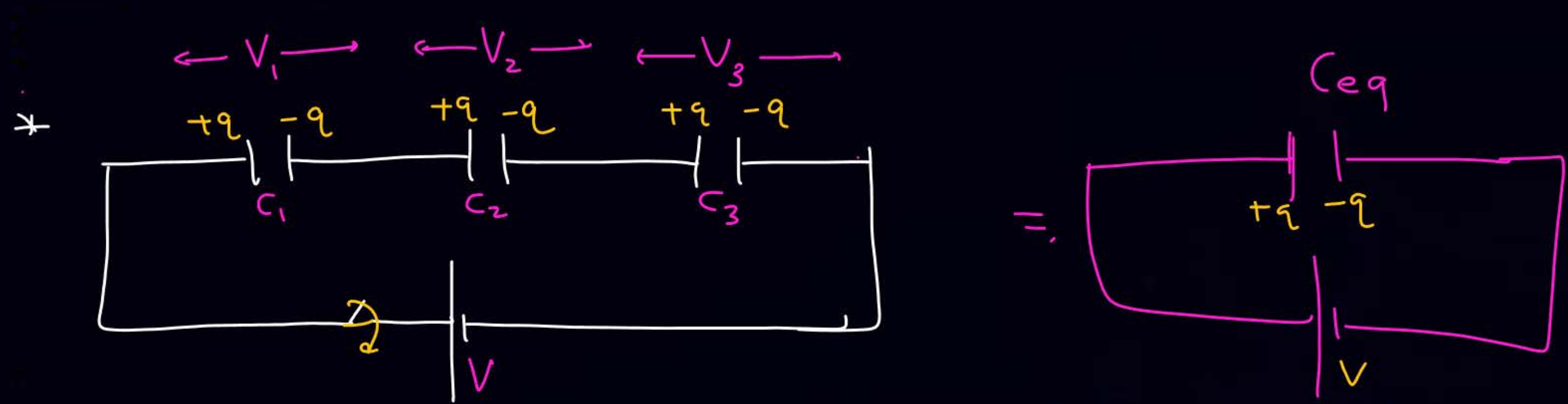

$$V = V_1 + V_2 + V_3 = \frac{q}{C_1} + \frac{q}{C_2} + \frac{q}{C_3} = \frac{q}{C_{eq}}$$
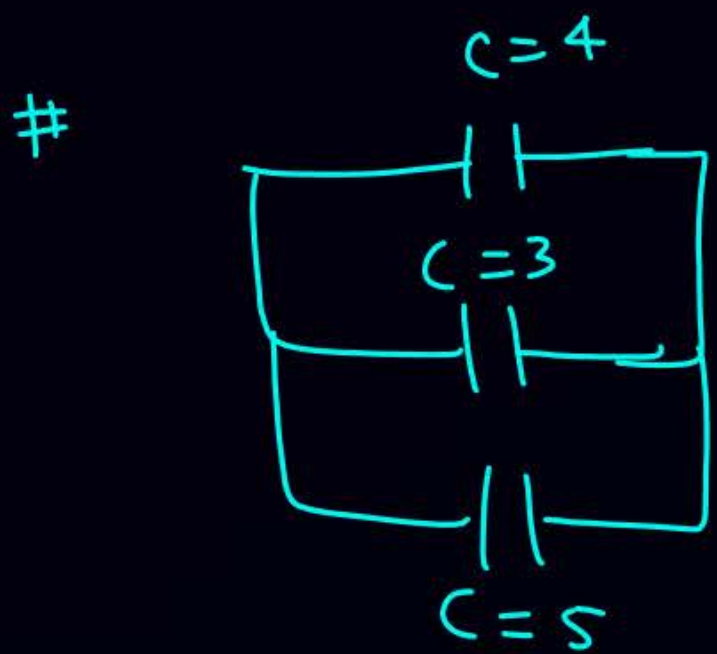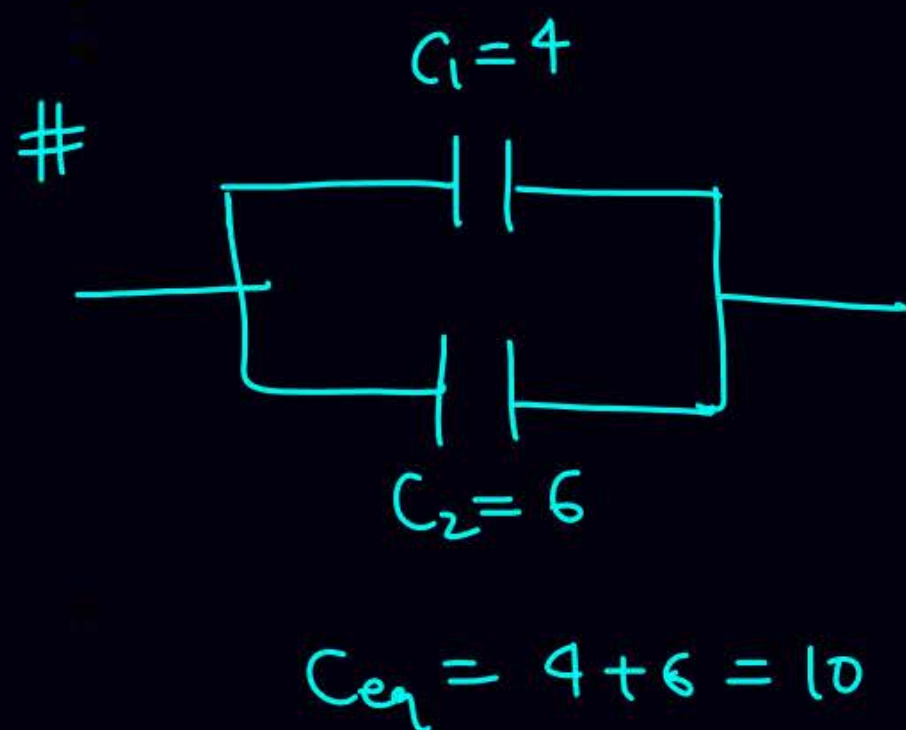
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$



ATDB.uno




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{C_1 + C_2}{C_1 C_2}$$


$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$



$$C_{eq} = \frac{18}{9} = 2$$

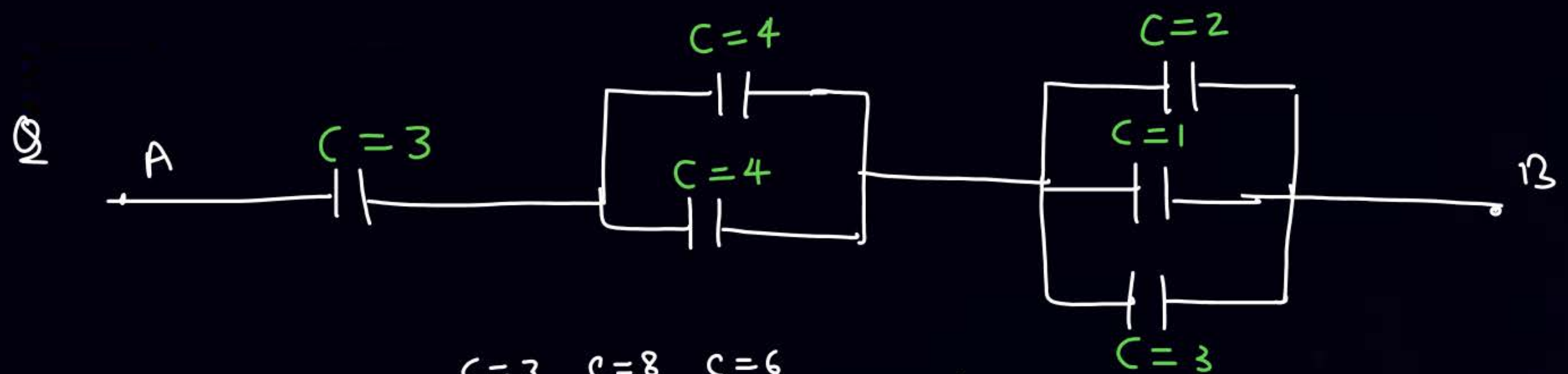

$(C_{eq})_{AB} = ?$

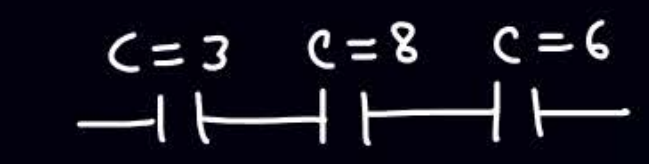



$$C_{eq} = \frac{2 \times 8}{2 + 8} = 1.6$$

ATDB.uno


Same

Q

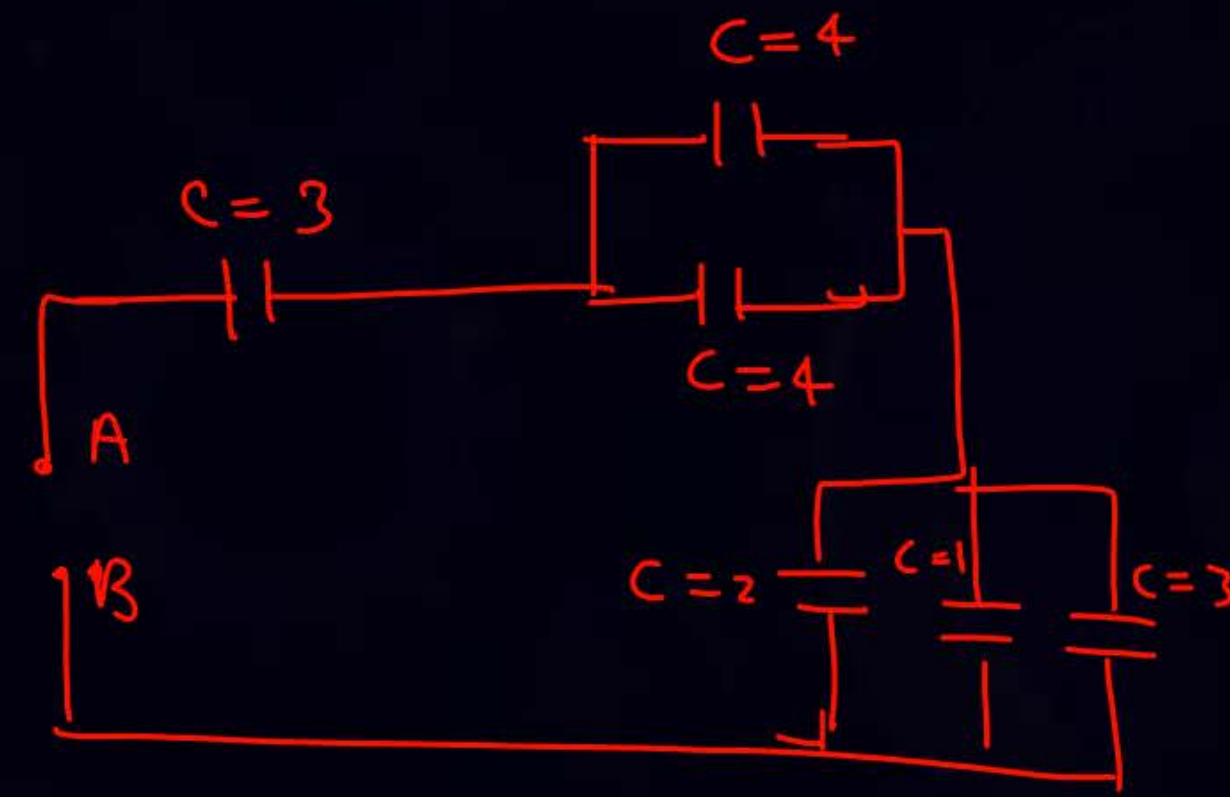


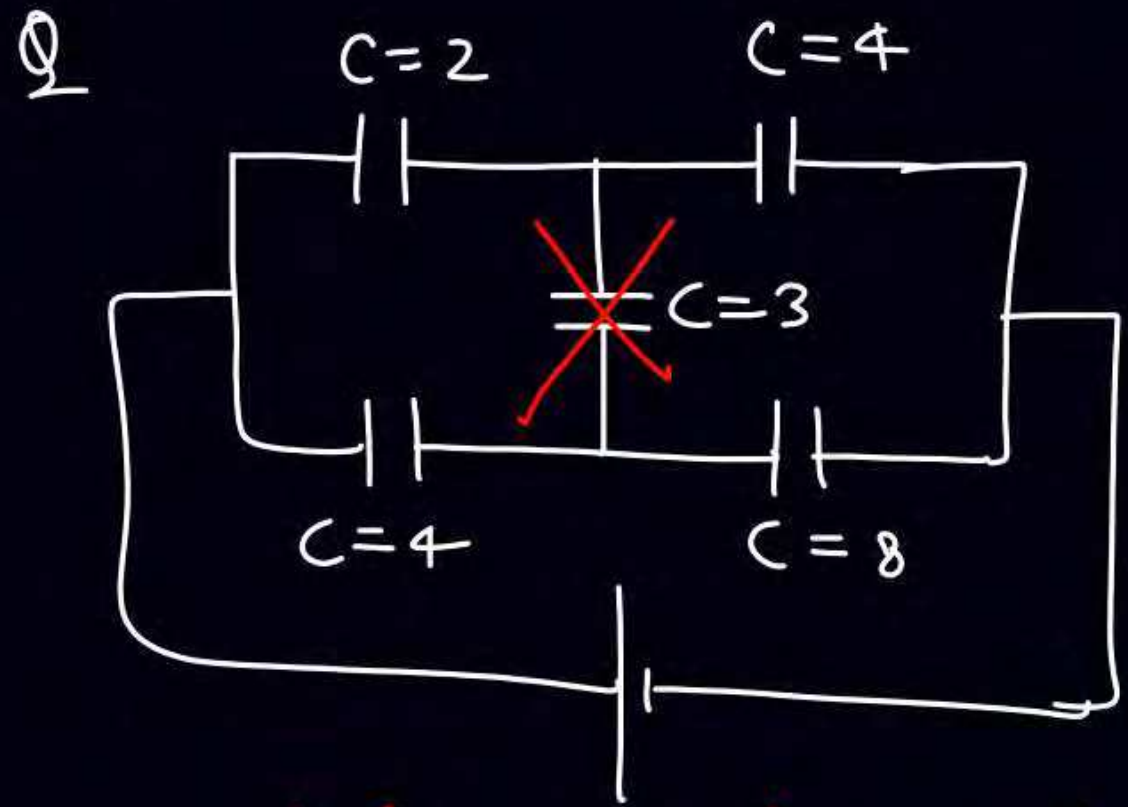

Balance wheent stone ✓

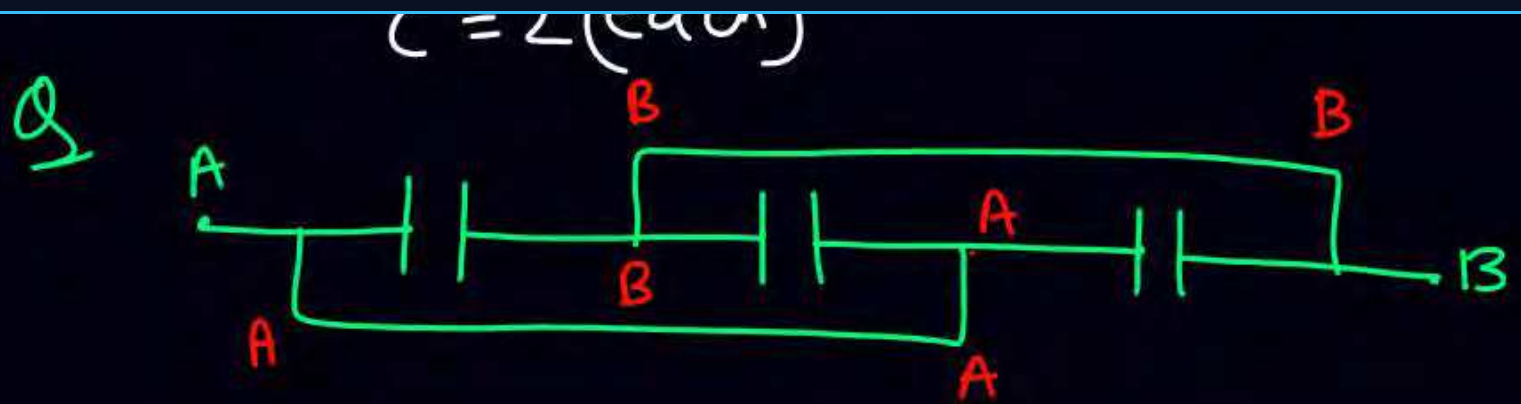


$C_{AB} = ?$

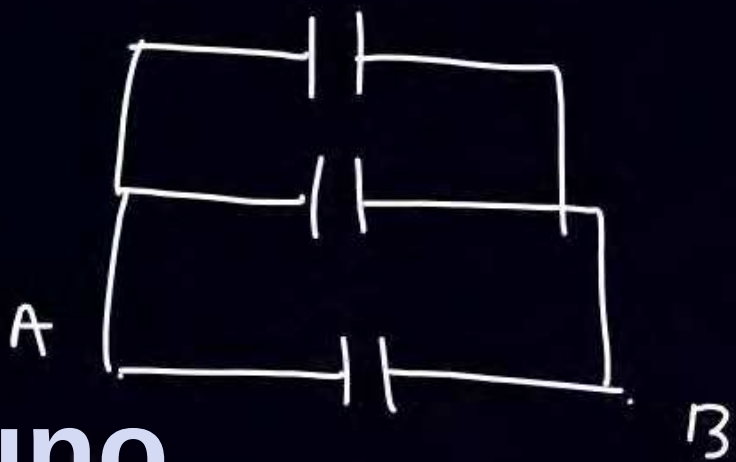


$C_{AB} = 2 + 2 + 2$

ATDB.uno




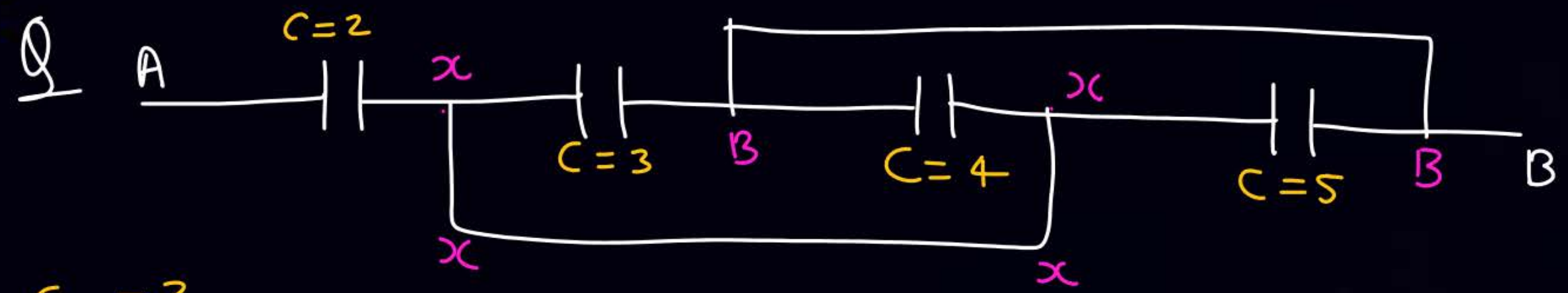


$C_{AB} = ?$

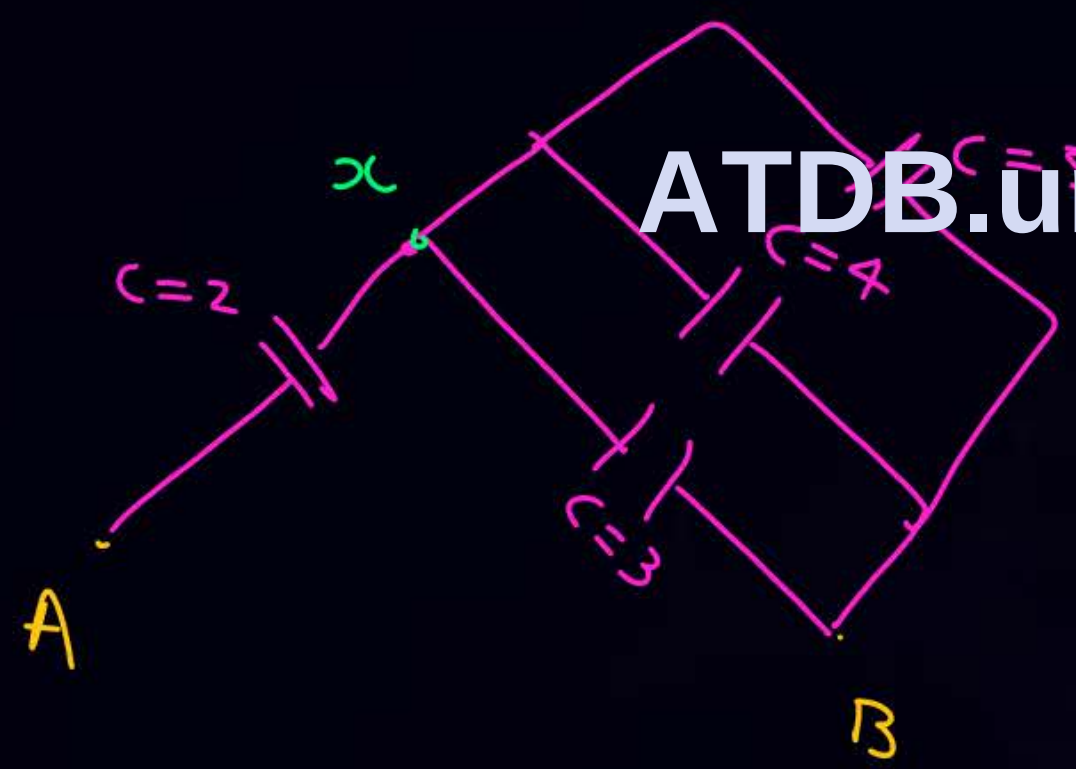


ATDB.uno

$C_{AB} = \frac{24}{14}$

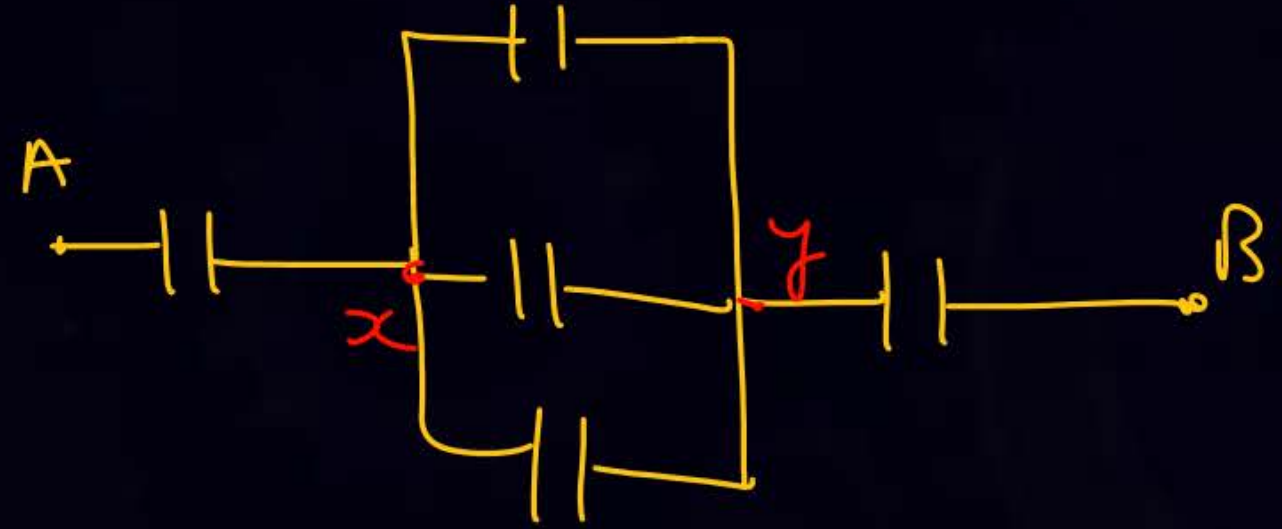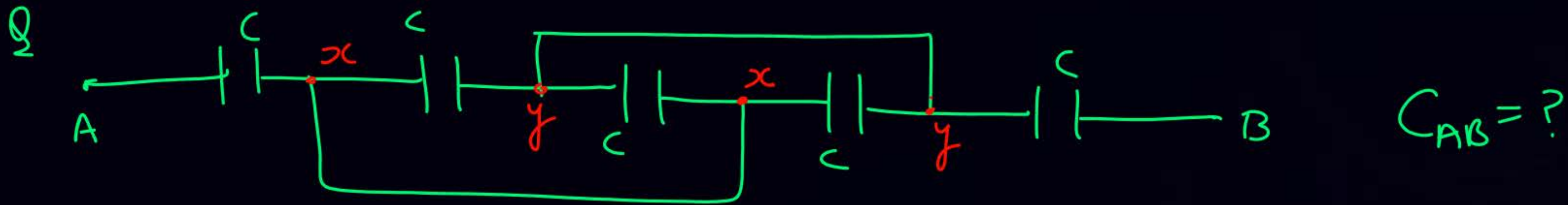



Q

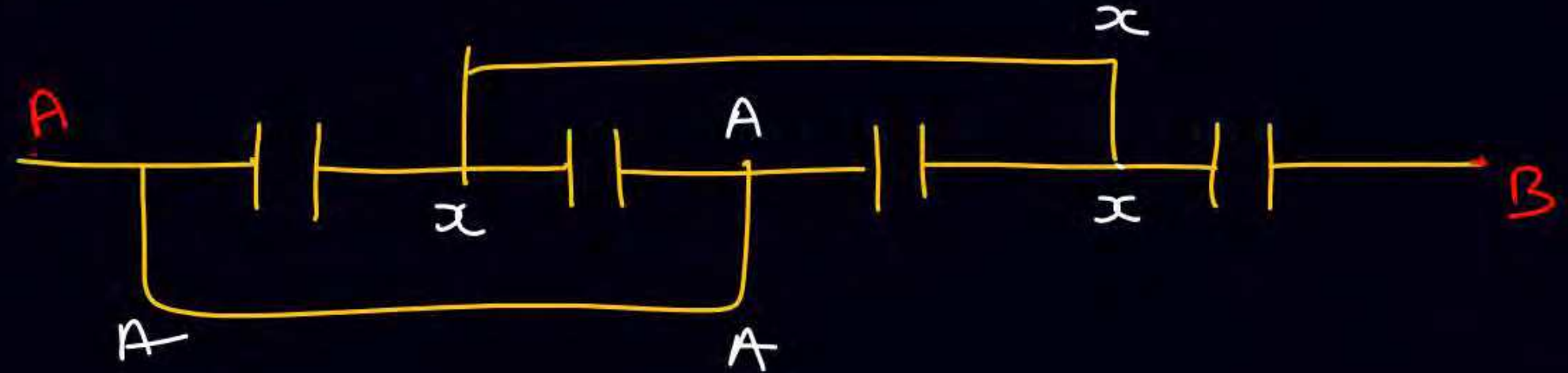

ATDB.uno

$$C_{eq} = \frac{3}{4} C$$



∞ Ladder


Q

A

B

∞

$C_{AB} = \infty$

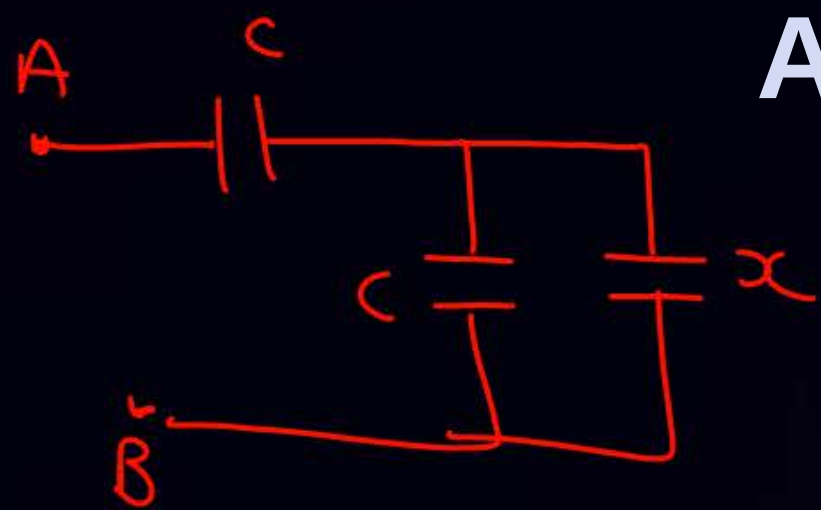

ATDB.uno


$$C_{AB} = \frac{(C+x) \cdot C}{(C+x) + C} = x$$


$$C^2 + xC = x(C+x) \Rightarrow C^2 + xC = xC + x^2 + Cx \Rightarrow C^2 = x^2$$


$$x^2 + xC - C^2 = 0$$

$$x = \frac{-C + \sqrt{5C^2}}{2}$$


(parallel plate cap.)

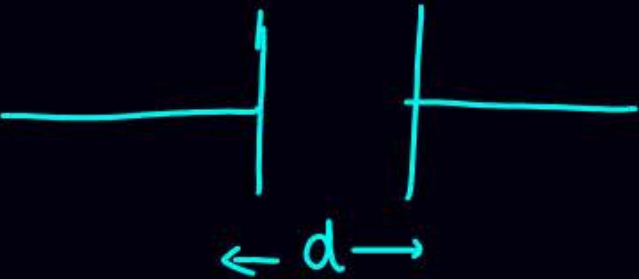
①  $C = \frac{A \epsilon_0}{d}$


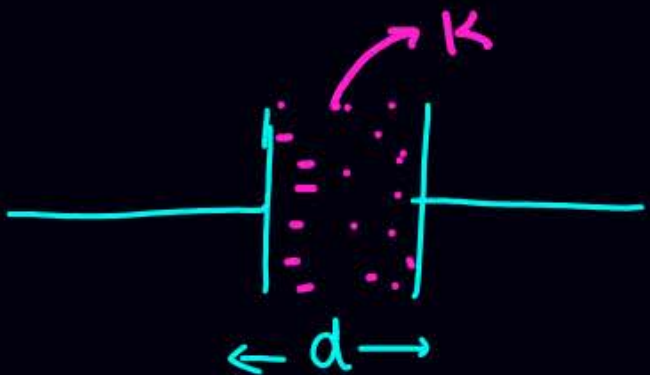
②  $C_{\text{now}} = \frac{A \epsilon_0 K}{d} = KC$

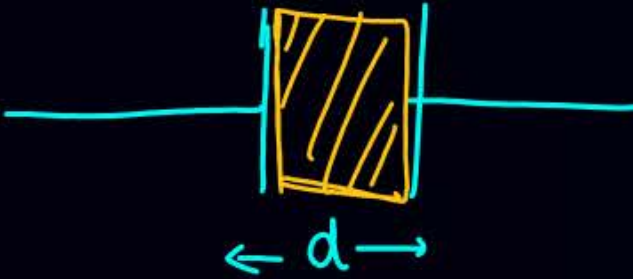③  $C_{\text{now}} = \frac{A \epsilon_0 K}{d} = KC$

ATDB.uno

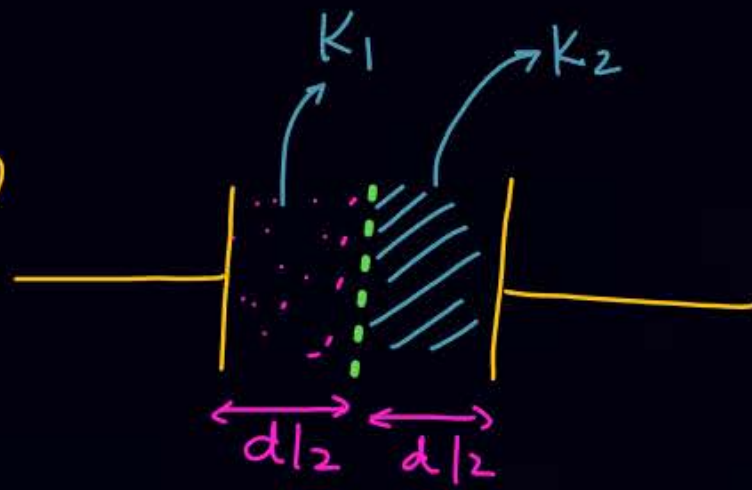④  $C_1 = \frac{A \epsilon_0 K_1}{(d/2)}$ $C_2 = \frac{A \epsilon_0 K_2}{(d/2)}$ $C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$

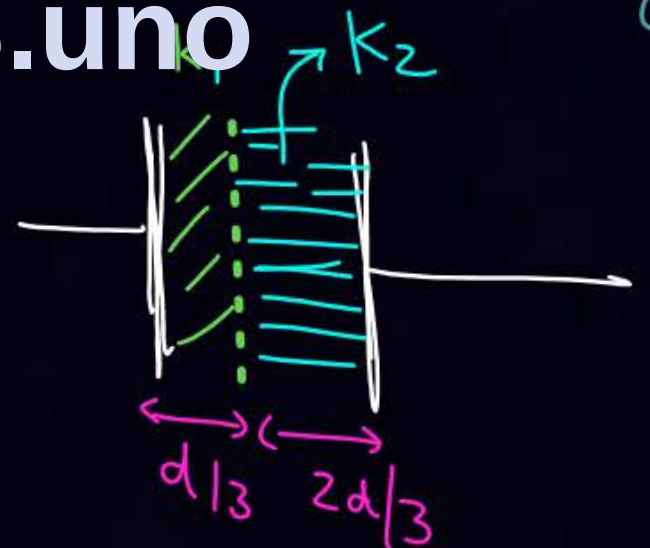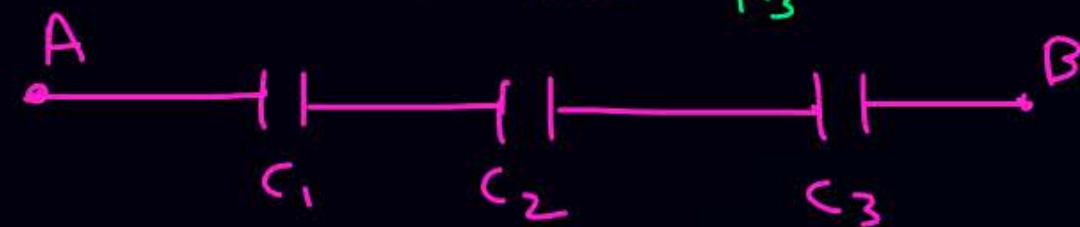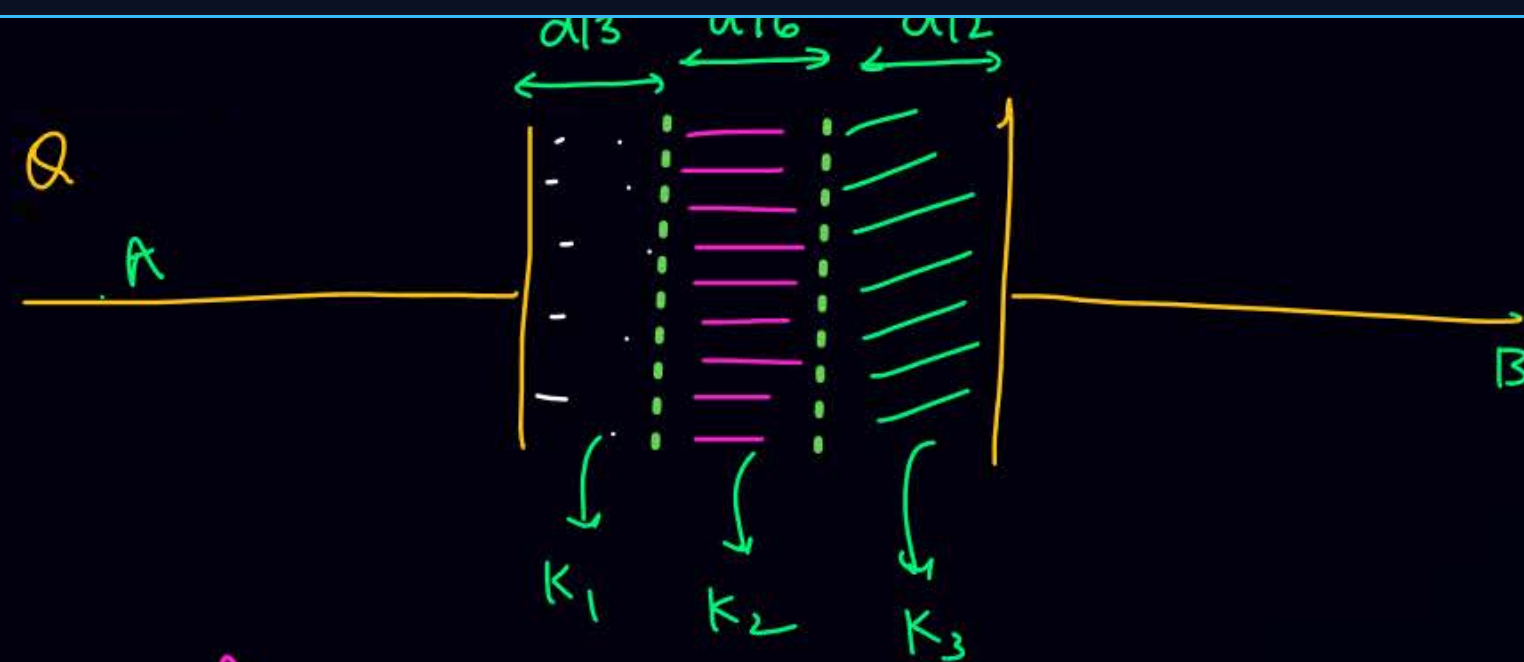⑤  $C_1 = \frac{A \epsilon_0 K_1}{d/3}$ $C_2 = \frac{A \epsilon_0 K_2}{2d/3}$




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$C_1 = \frac{A \epsilon_0 K_1}{d/3}$$

$$C_2 = \frac{A \epsilon_0 K_2}{d/6}$$

$$C_3 = \frac{A \epsilon_0 K_3}{d/2}$$

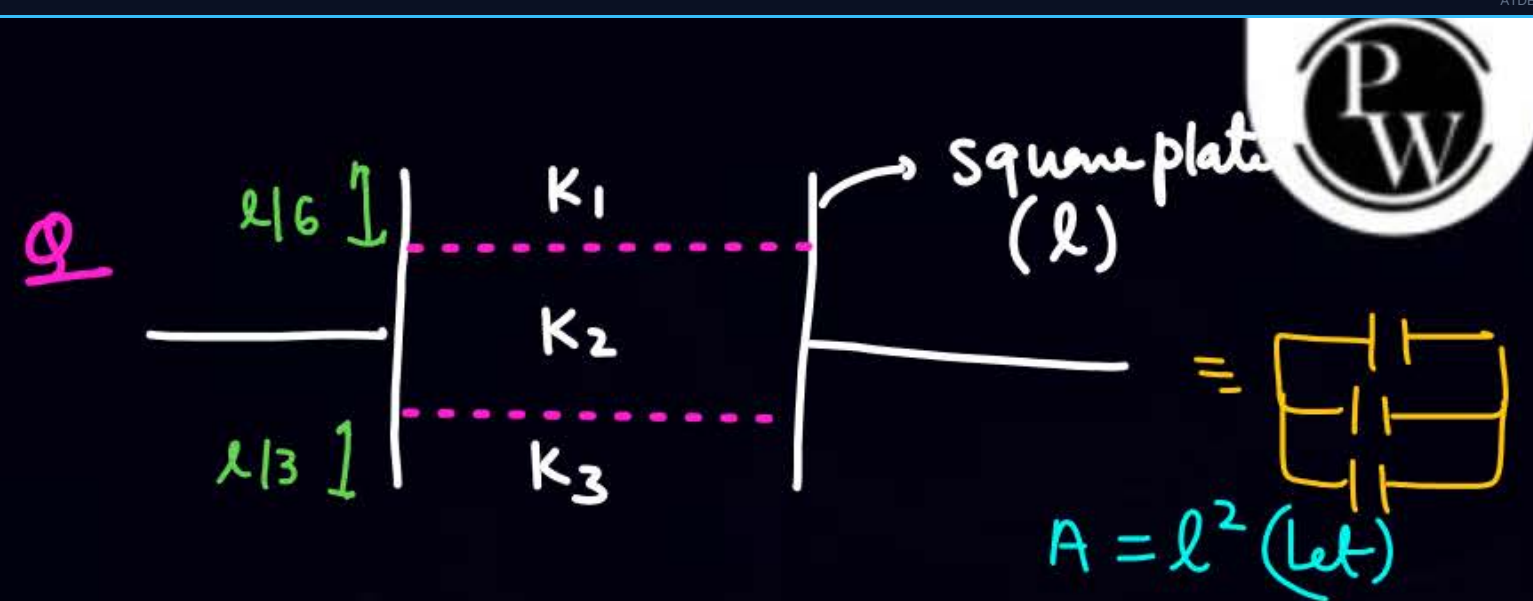

$$C_{eq} = C_1 + C_2 + C_3$$


$$= \frac{\frac{A}{6} \epsilon_0 K_1}{d} + \frac{\frac{A}{2} \epsilon_0 K_2}{d} + \frac{\frac{A}{3} \epsilon_0 K_3}{d}$$



$$C_{eq} = C_1 + C_2 = \frac{(A/2) \epsilon_0 K_1}{d} + \frac{(A/2) \epsilon_0 K_2}{d}$$



Ques


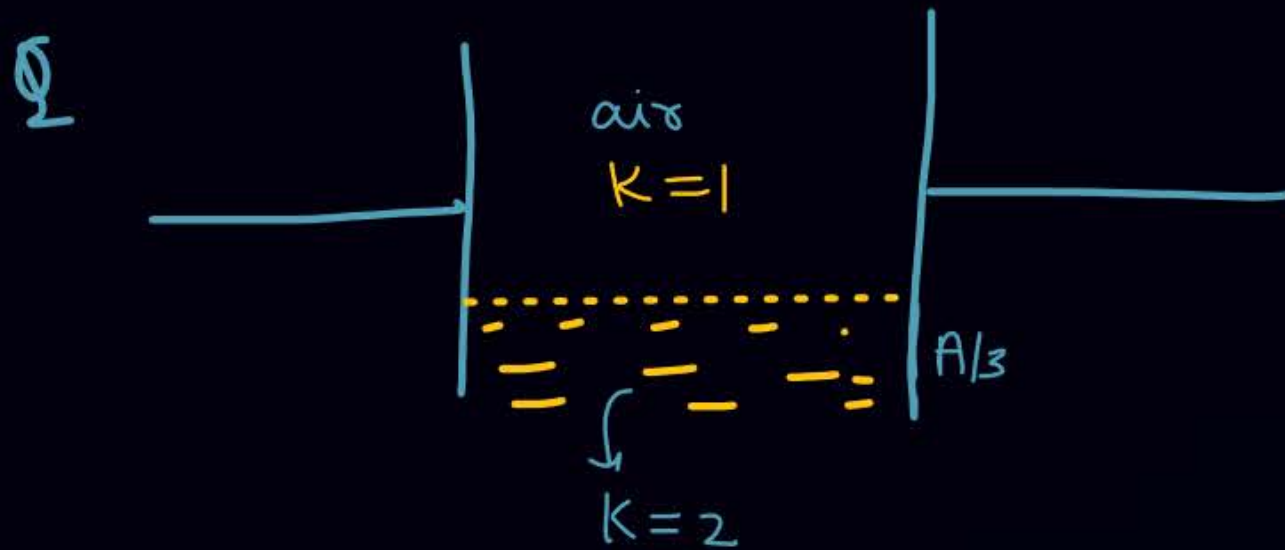


$$C_{eq} = C_1 + C_2 = \frac{\frac{2A}{3} \epsilon_0}{d} + \frac{\left(\frac{A}{3}\right) \epsilon_0 \times 2}{d}$$

ATDB.uno

कैराम Qus जेए

Q

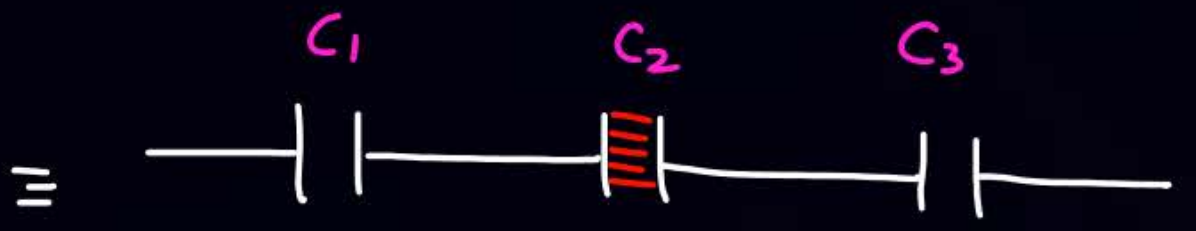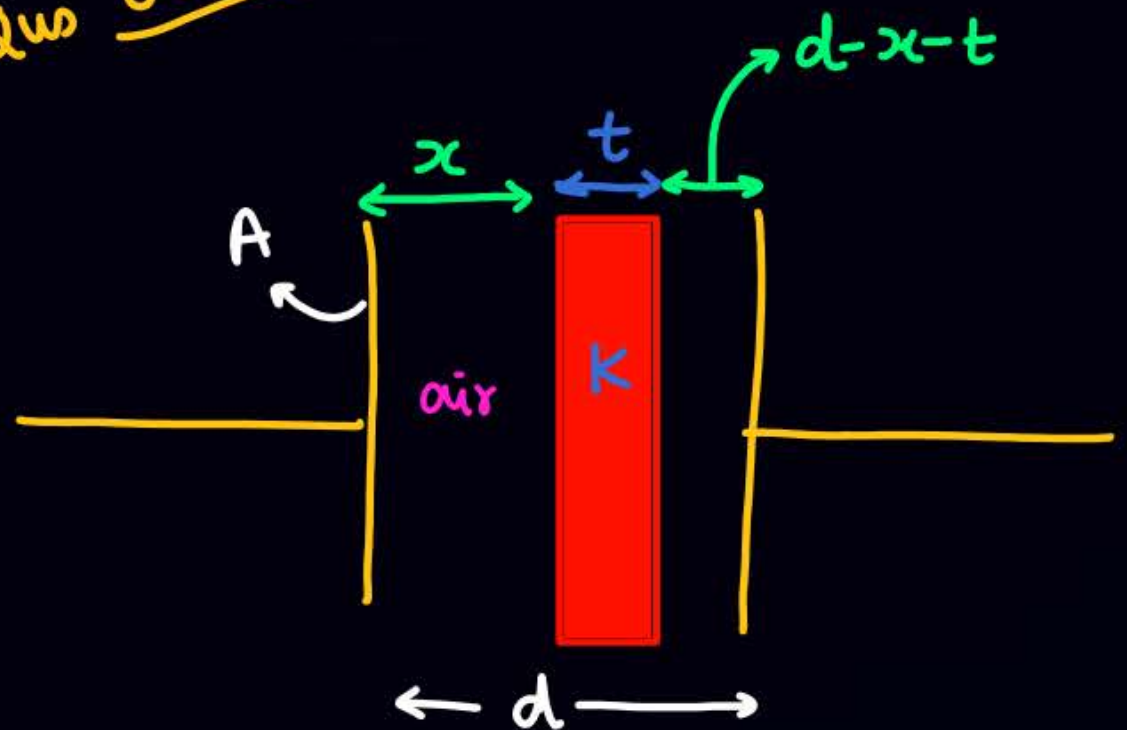


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

ATDB.uno

$$\frac{1}{C_{eq}} = \frac{1}{\left(\frac{A\epsilon_0}{x}\right)} + \frac{1}{\frac{A\epsilon_0 K}{t}} + \frac{1}{\frac{A\epsilon_0}{(d-x-t)}} = \frac{1}{A\epsilon_0} \left[\cancel{x} + \frac{t}{K} + d - \cancel{x} - t \right]$$
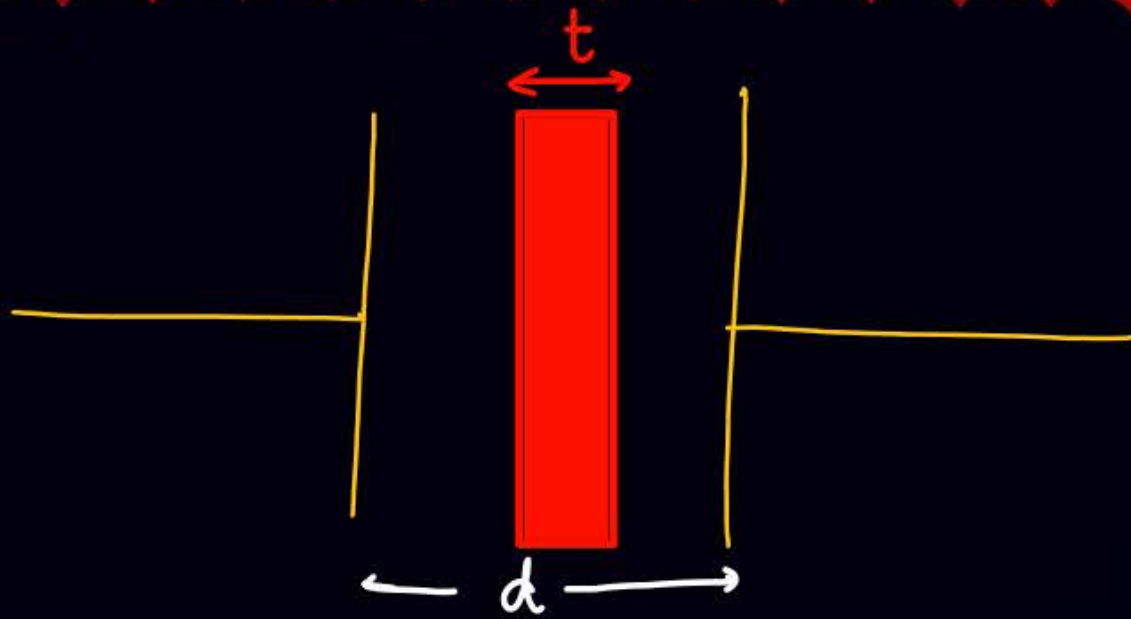
$$C_{eq} = \frac{A\epsilon_0}{\frac{t}{K} + d - t} = \frac{A\epsilon_0}{d - t \left(1 - \frac{1}{K}\right)}$$



$$C = \frac{A\epsilon_0}{d - t\left(1 - \frac{1}{k}\right)}$$

ATDB.uno


Solⁿ

$$\frac{C_{\text{new}}}{\left(\frac{A\epsilon_0}{d}\right)} = \frac{C_{\text{new}}}{C_{\text{old}}} = \frac{12}{12 - 3 + 1} = \frac{12}{10} = \frac{6}{5}$$

Q Between the parallel plate capacitor of capacitance C , (plate area A & distance b/w plate is d) a dielectric slab of dielectric const $k=3$ is inserted as shown in diagram.

If thickness of slab is $\frac{d}{4}$ find

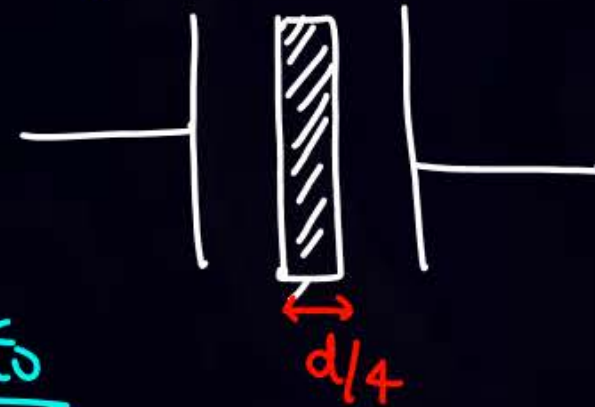Ratio of $\frac{C_{\text{new}}}{C_{\text{old}}} = ?$




$$C_{\text{new}} = \frac{A\epsilon_0}{d - \frac{d}{4}\left(1 - \frac{1}{3}\right)} = \frac{A\epsilon_0}{d\left[1 - \frac{1}{4} + \frac{1}{12}\right]}$$



ATDB.uno
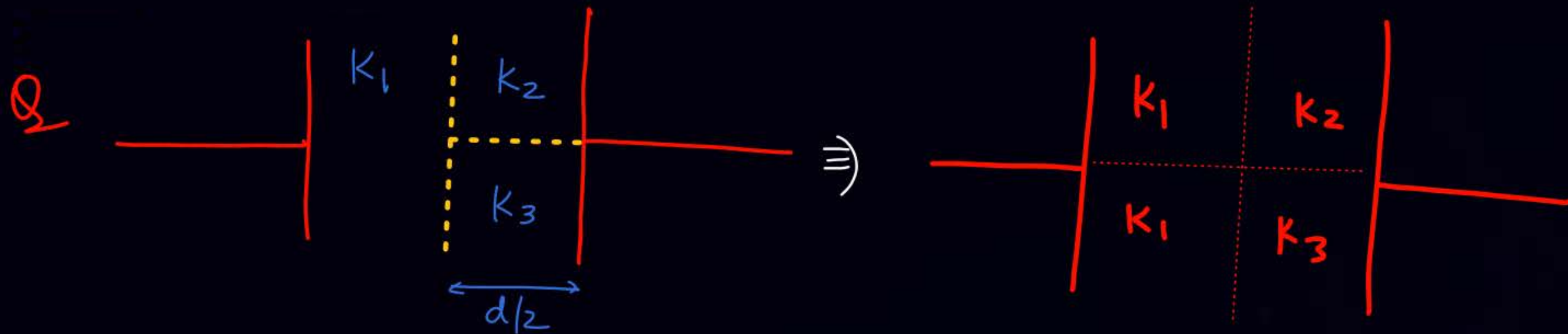
$$C_1 = \frac{(A/2) \epsilon_0 k_1}{d/2}$$
$$C_2 = \frac{(A/2) \epsilon_0 k_2}{d/2}$$
$$C_3 = \frac{(A/2) \epsilon_0 k_3}{d}$$



ATDB.uno

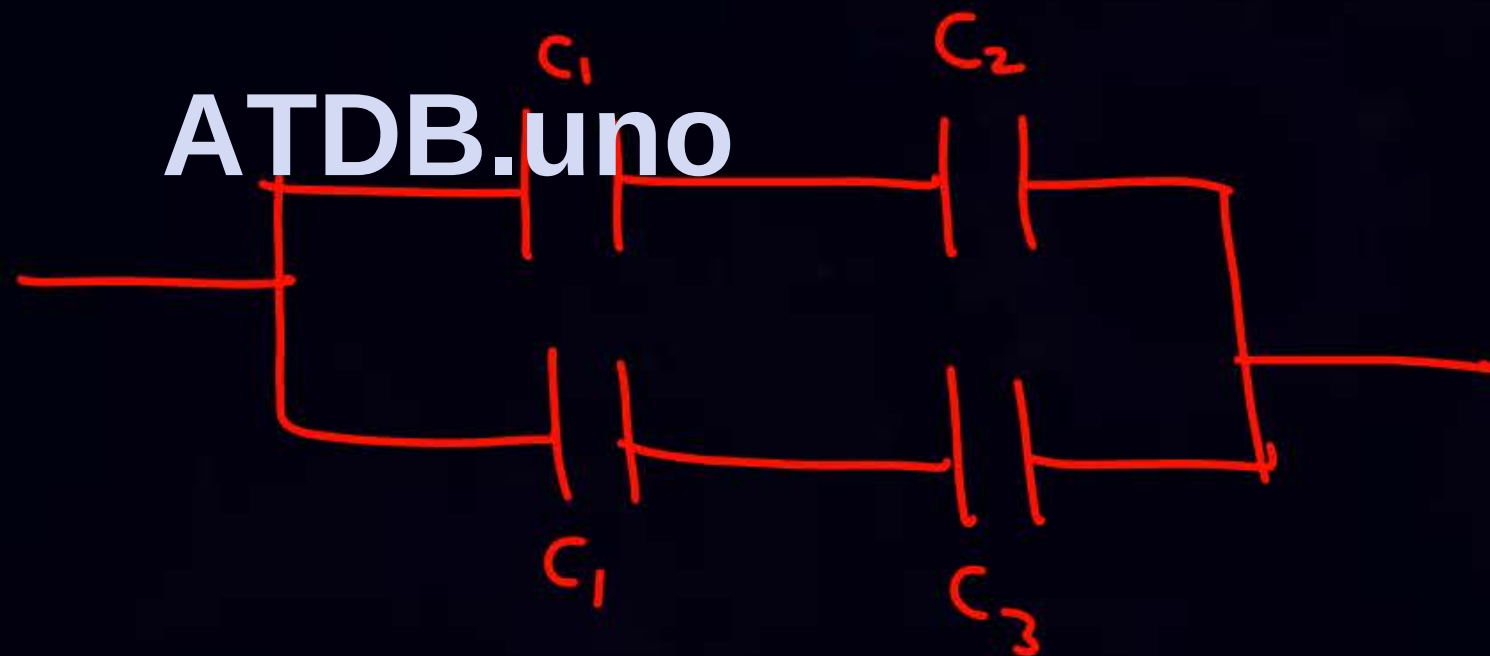
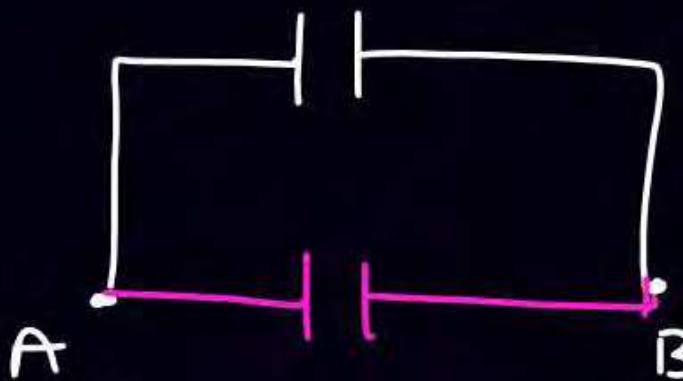
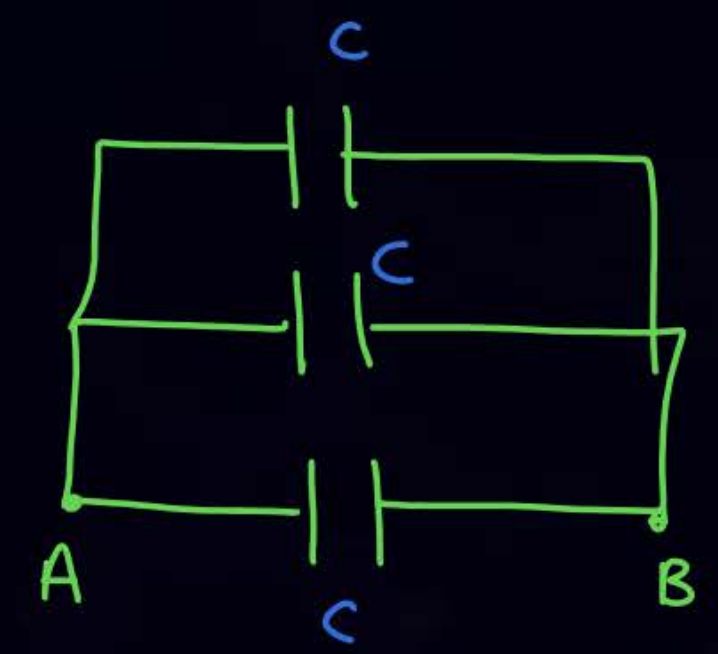
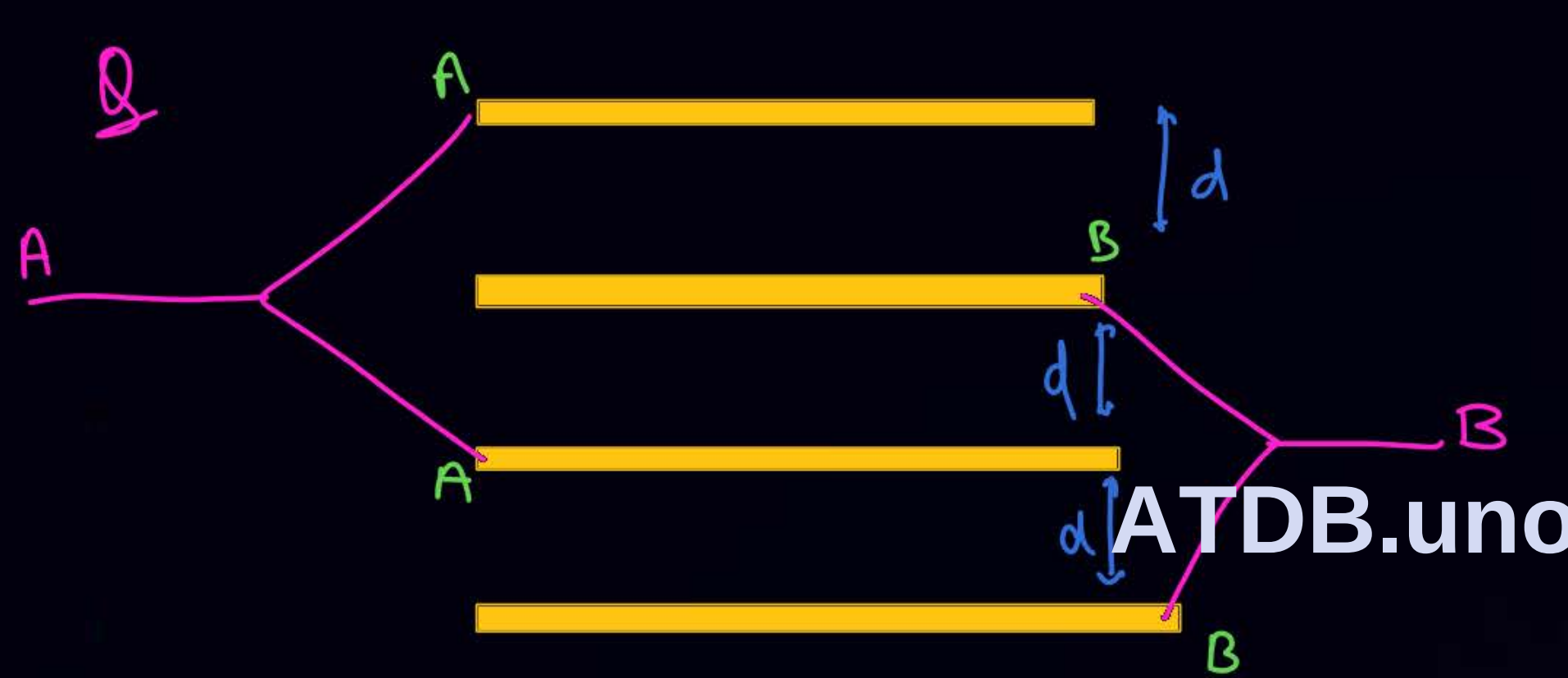


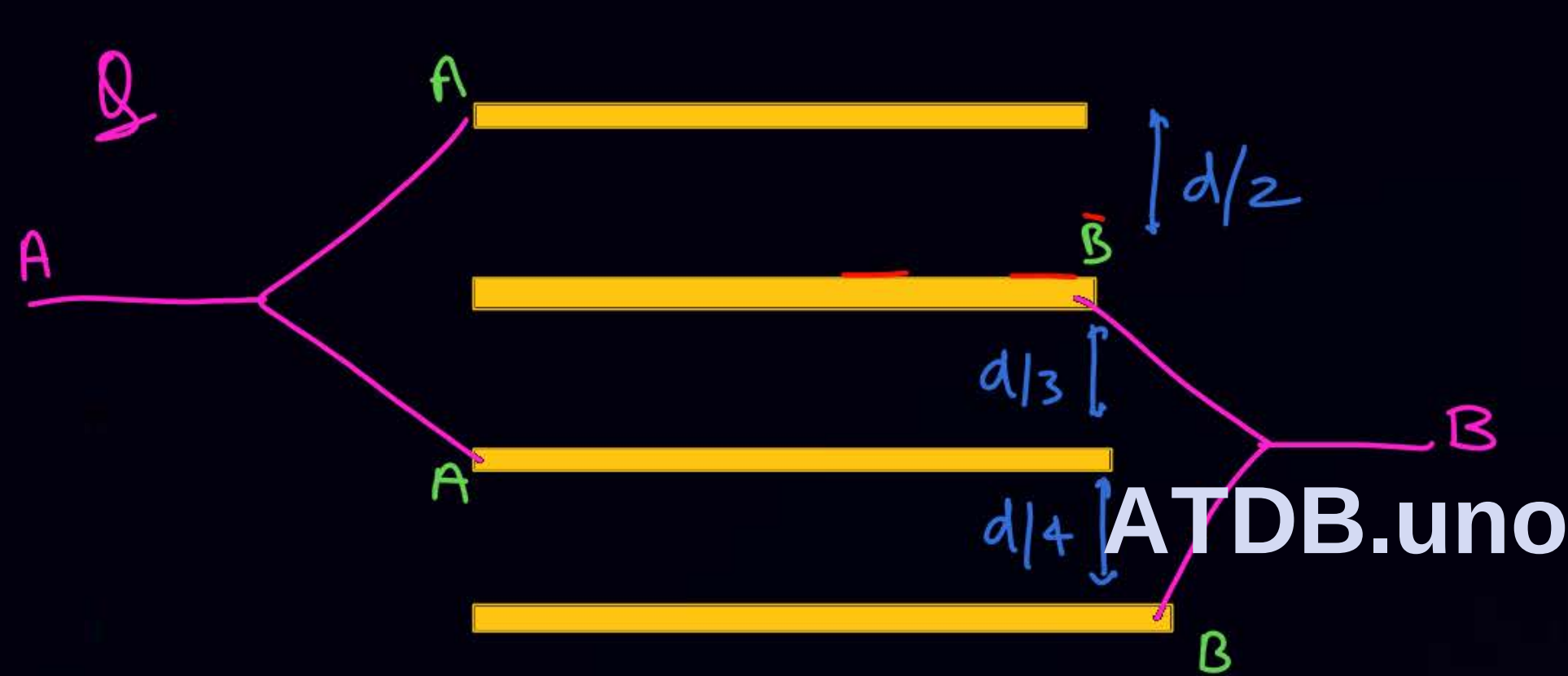


plate wale Ques








$$C = \frac{A\epsilon_0}{d}, \quad C_{eq} = 3C$$






$$C = \frac{A\epsilon_0}{d}$$

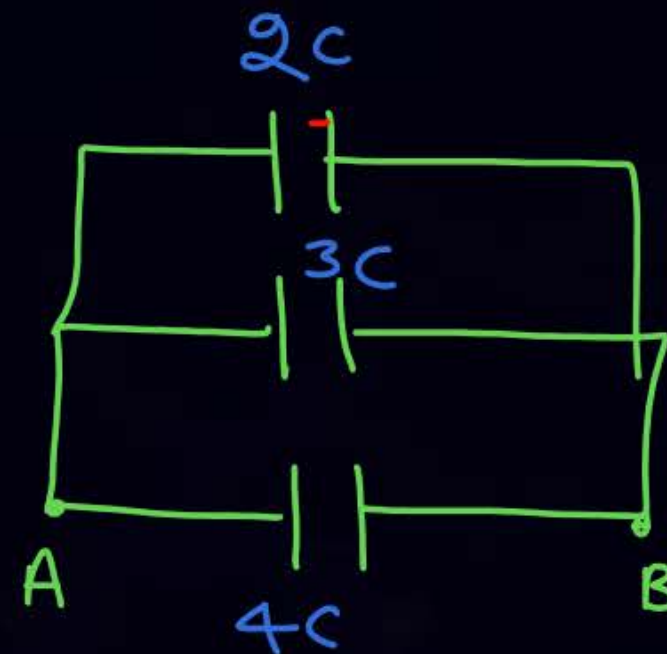

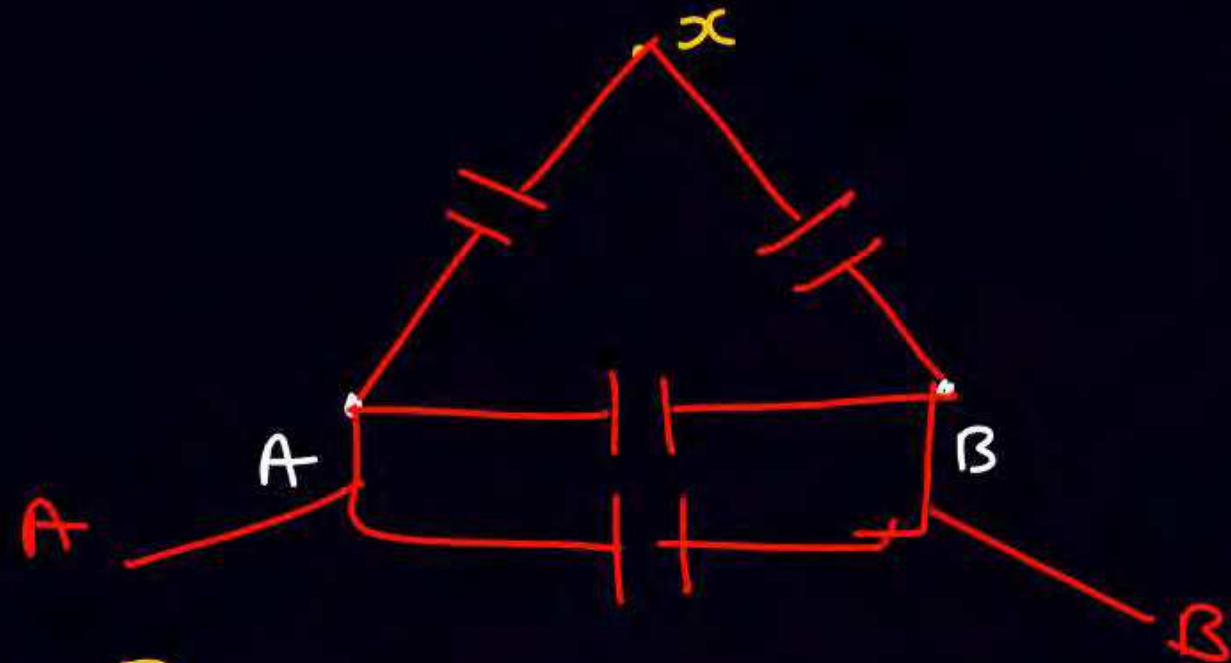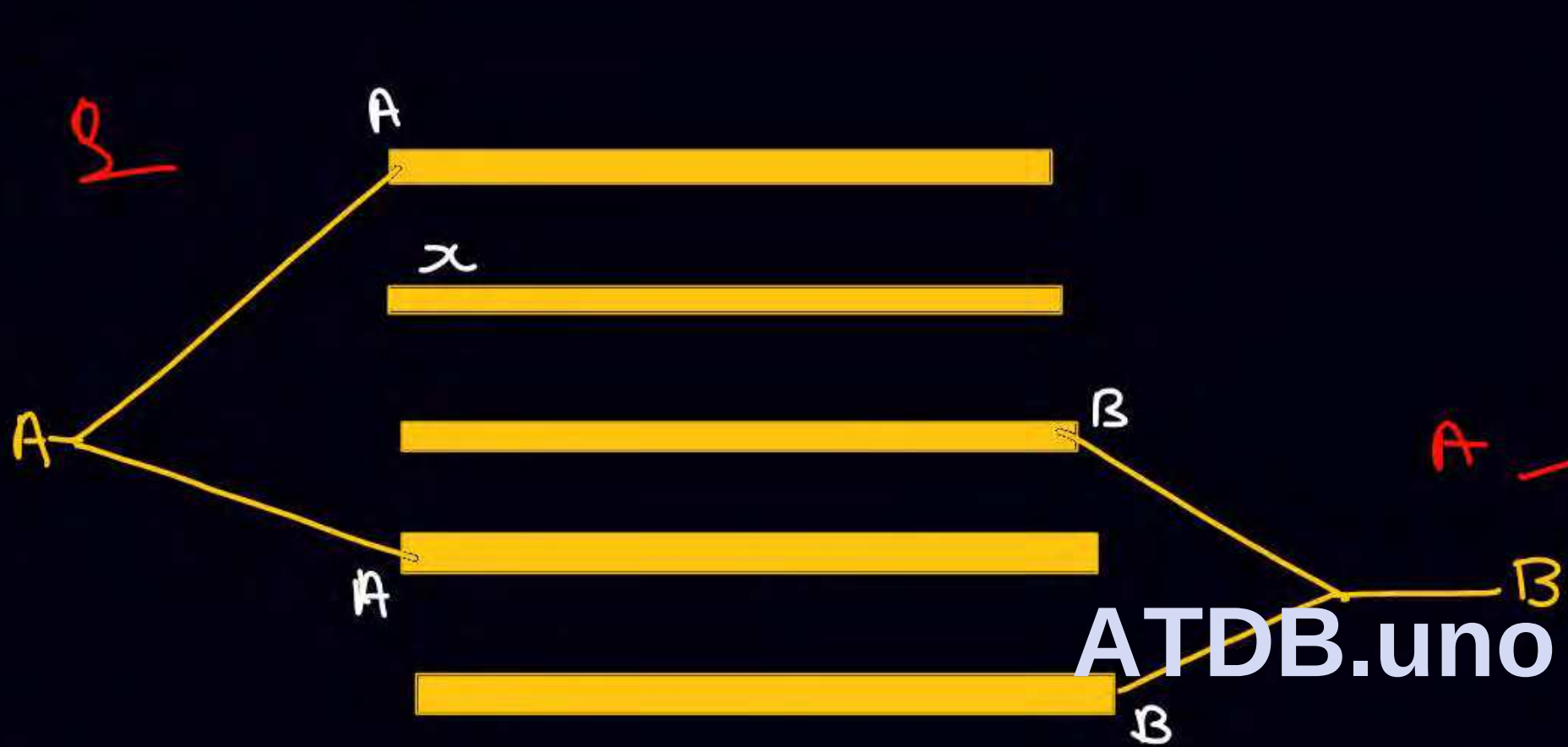
$$C = \frac{A\epsilon_0}{d}, \quad C_{eq} = 9C$$




ATDB.uno

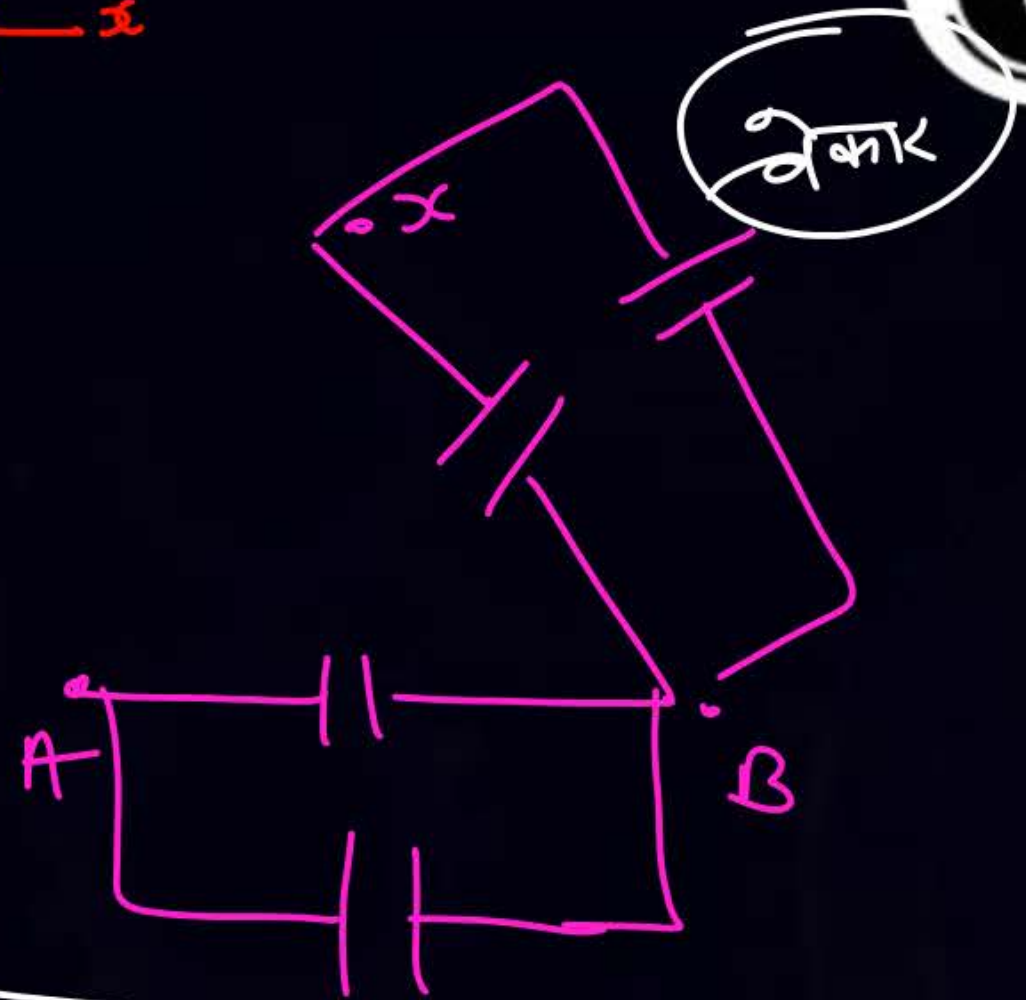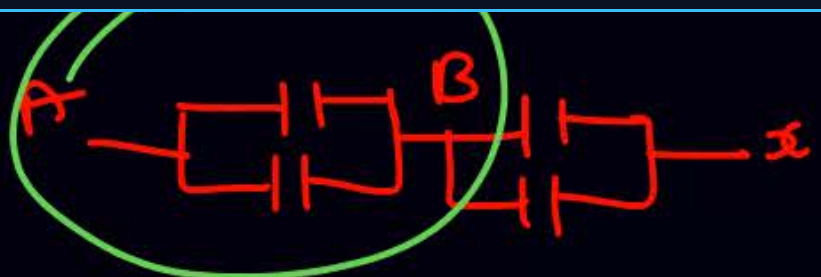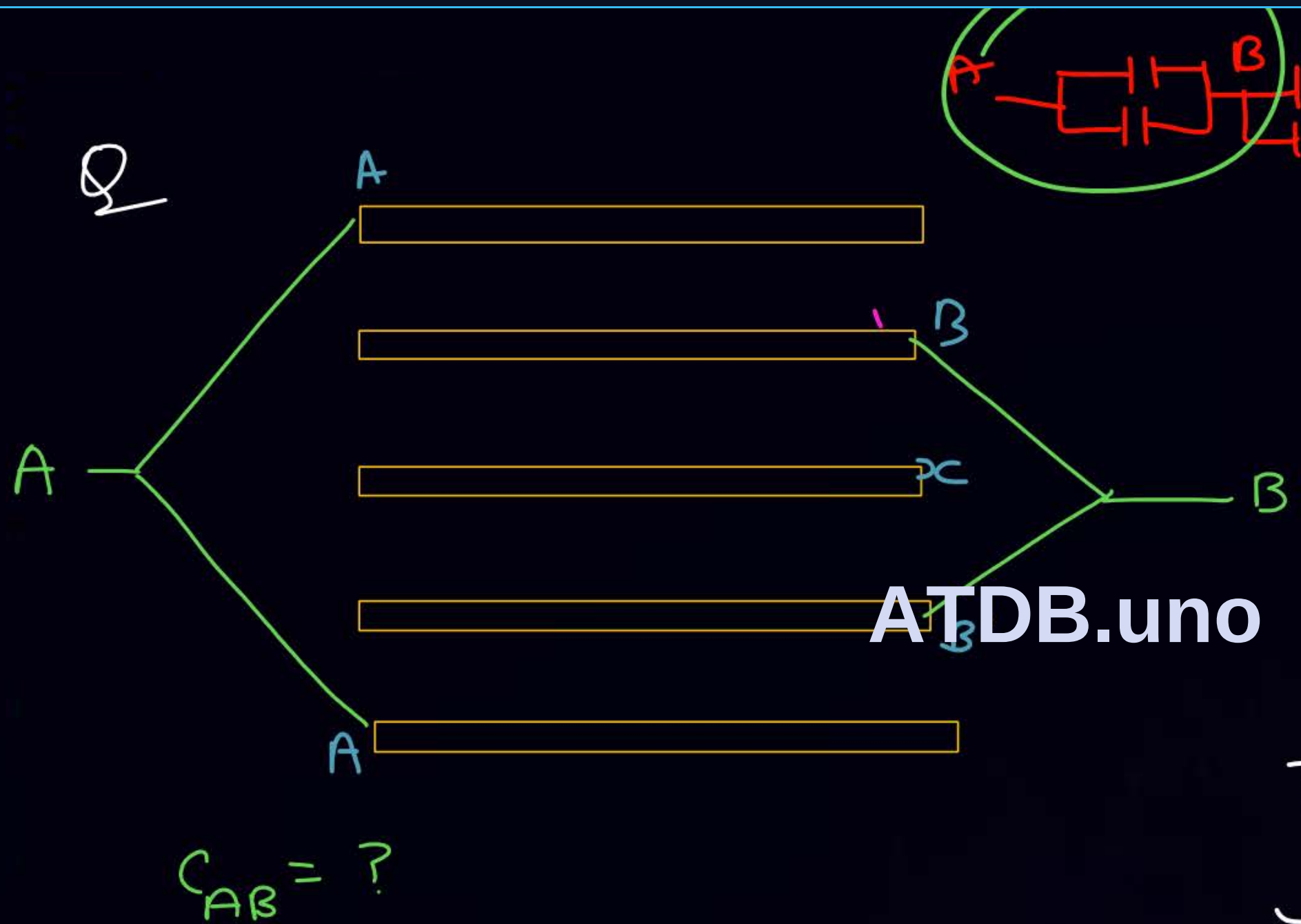

$C_{eq} = 2C$

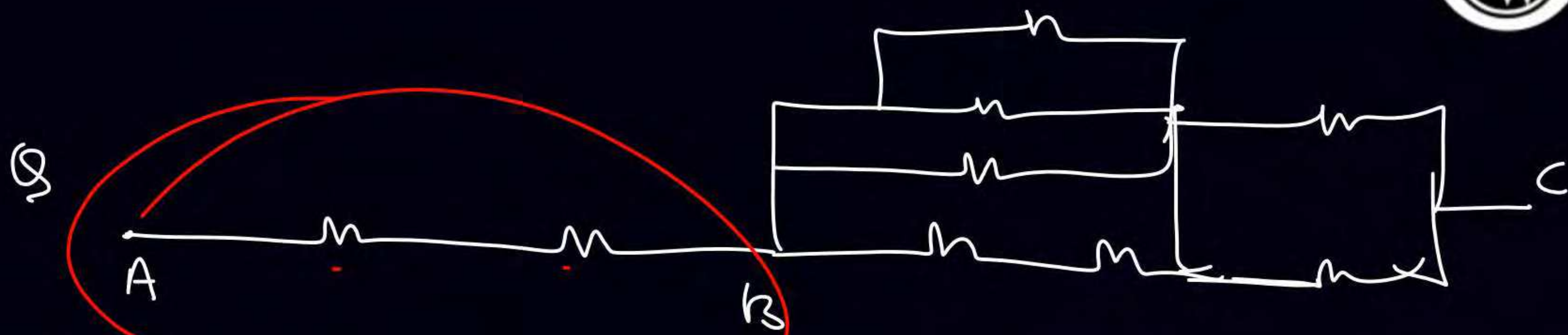


ATDB.uno

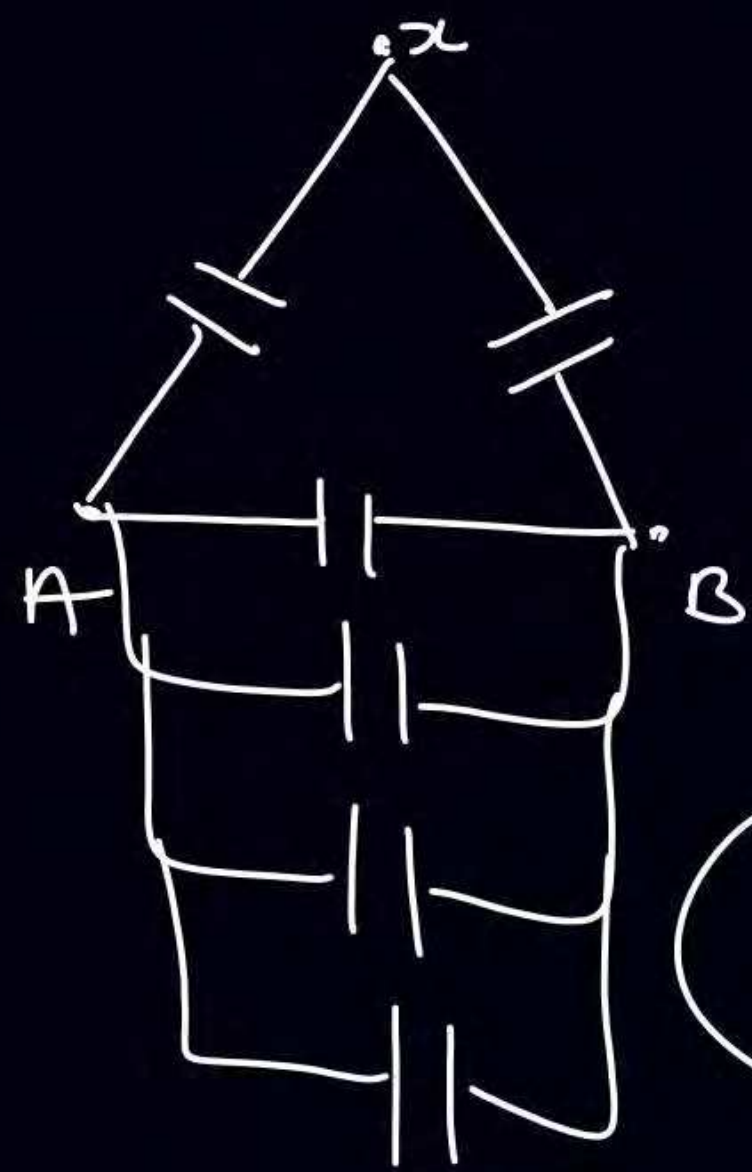



$C_{eq} = 4.5C$

ATDB.uno

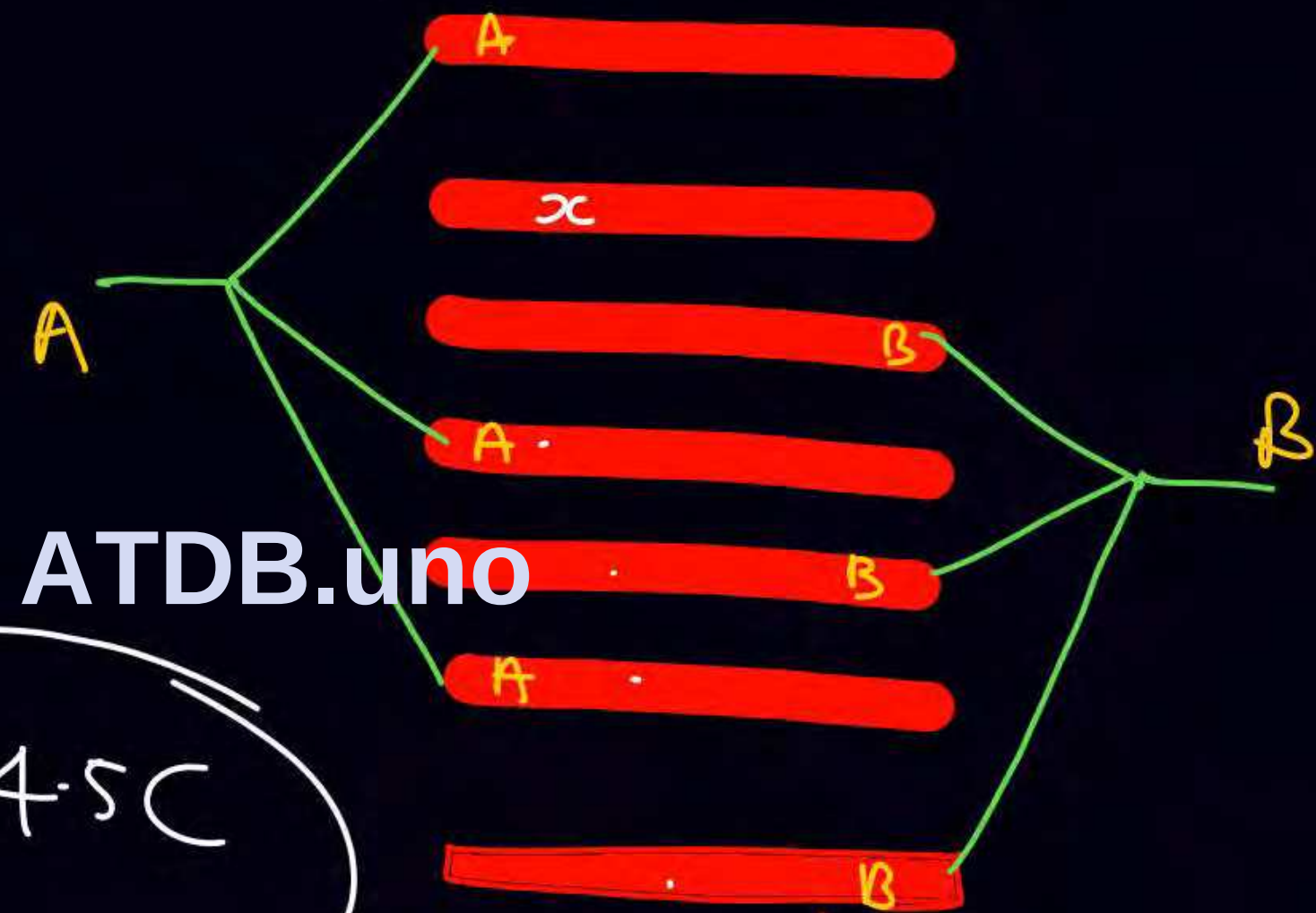


$\frac{A}{d} = C$

Q

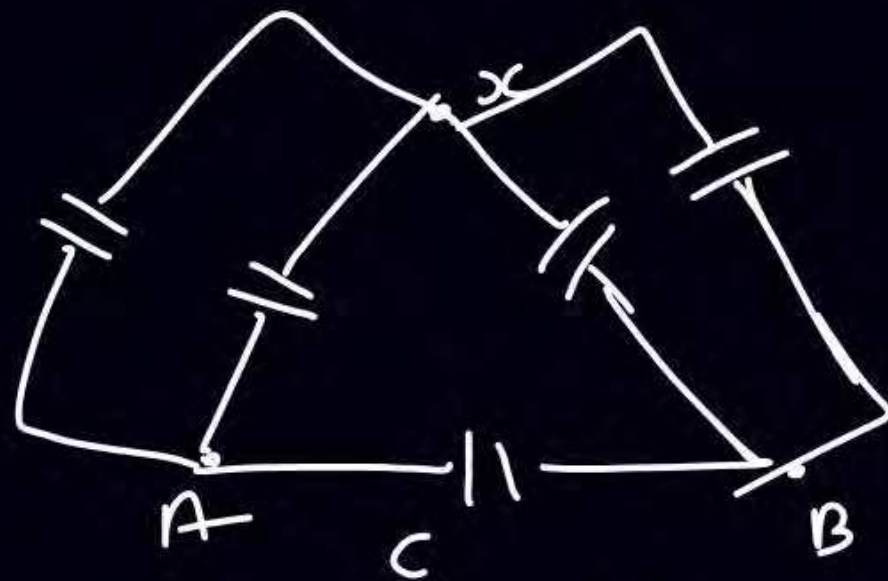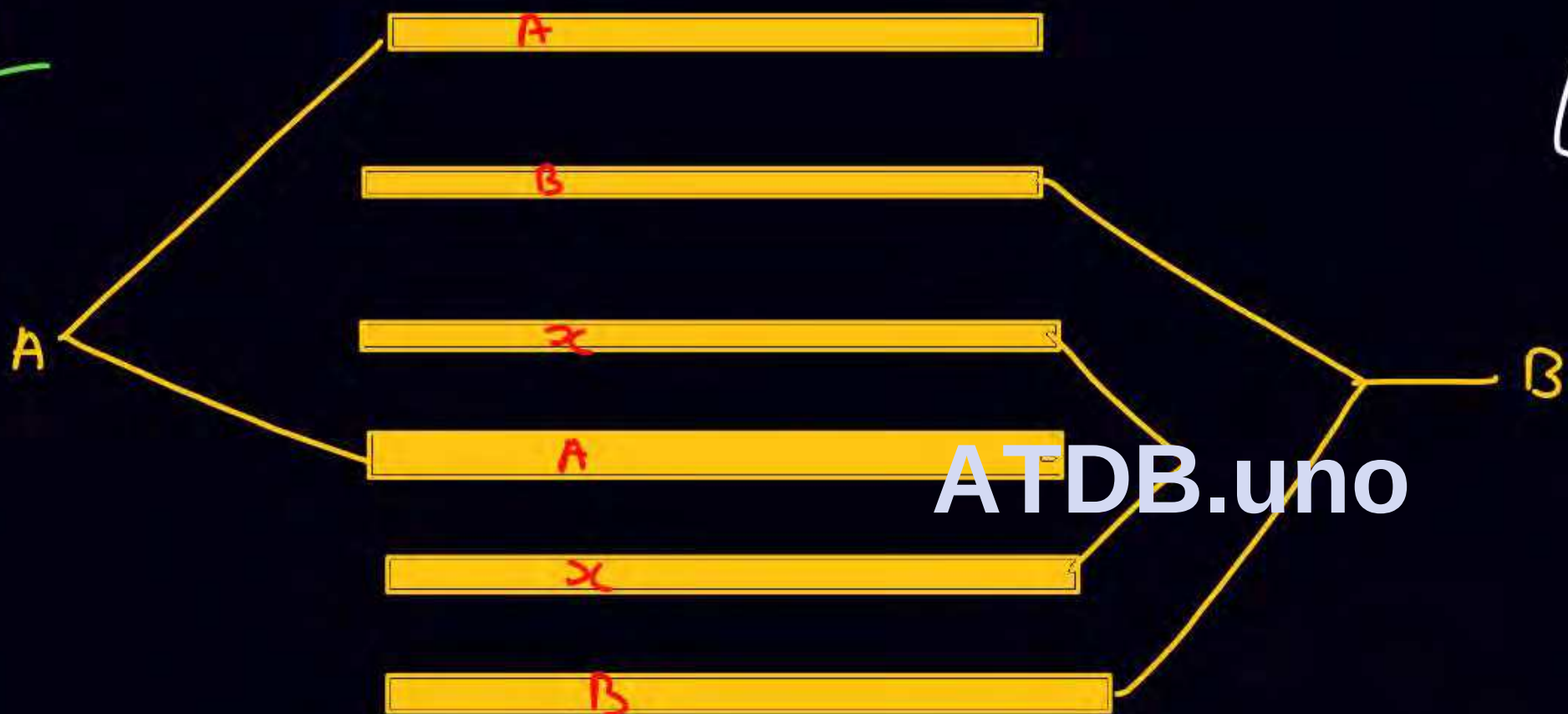

$$C_{eq} = 2C$$



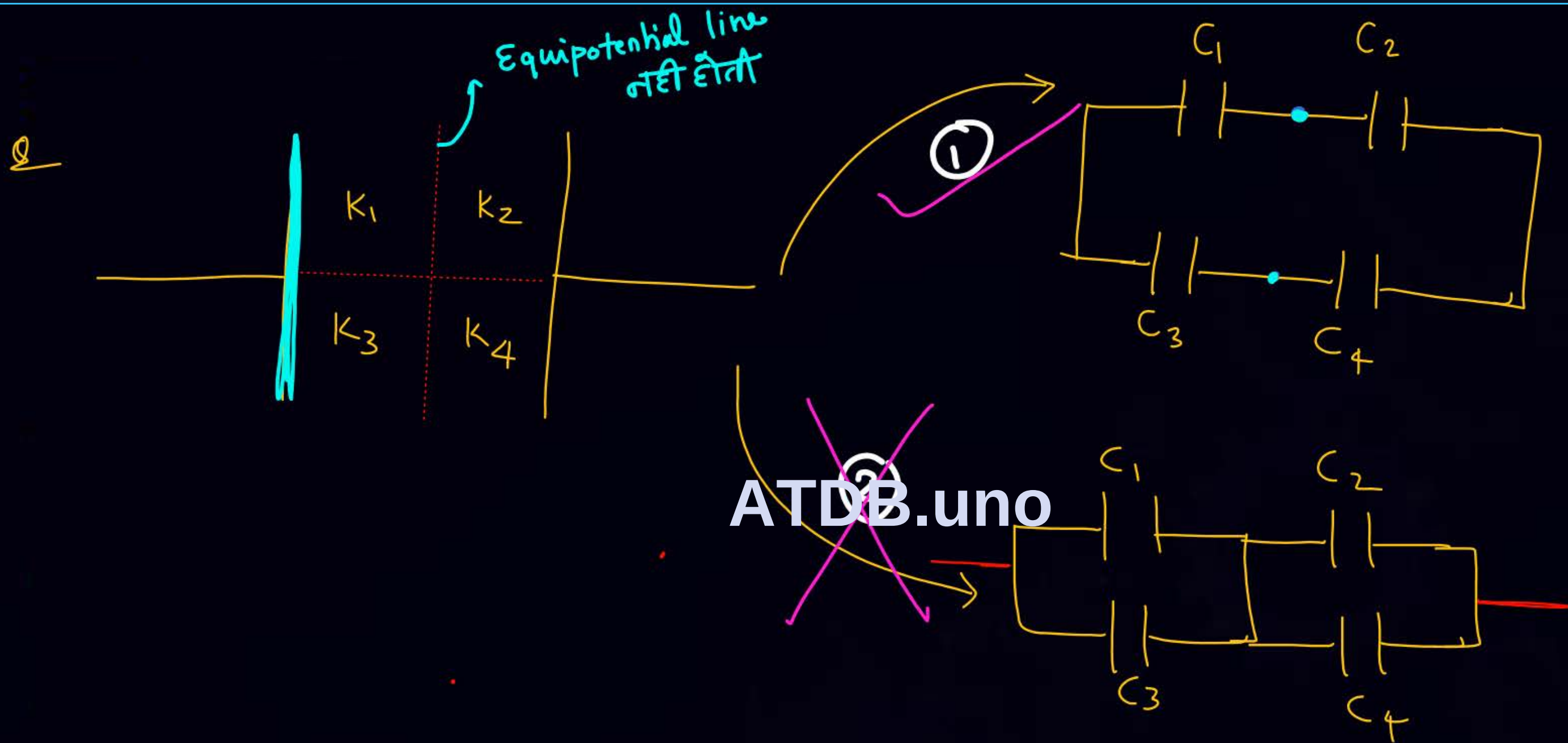



If two appliances with rating (w_1, V) & (w_2, V) are connected to 'V'

① In parallel $\Rightarrow$ Total power dissipated $= w_1 + w_2$

② In series $\Rightarrow$ " " " " $= w_{\text{net}}$ then $\frac{1}{w_{\text{net}}} = \frac{1}{w_1} + \frac{1}{w_2}$

ATDB.uno

xx
$$P_{\text{net}} = \frac{V^2}{R_{\text{eq}}}$$


Dissipated

,
$$P_{\text{net}} = i^2 R_{\text{eq}}$$

Dissipated



Q find $R_{eq} = ?$

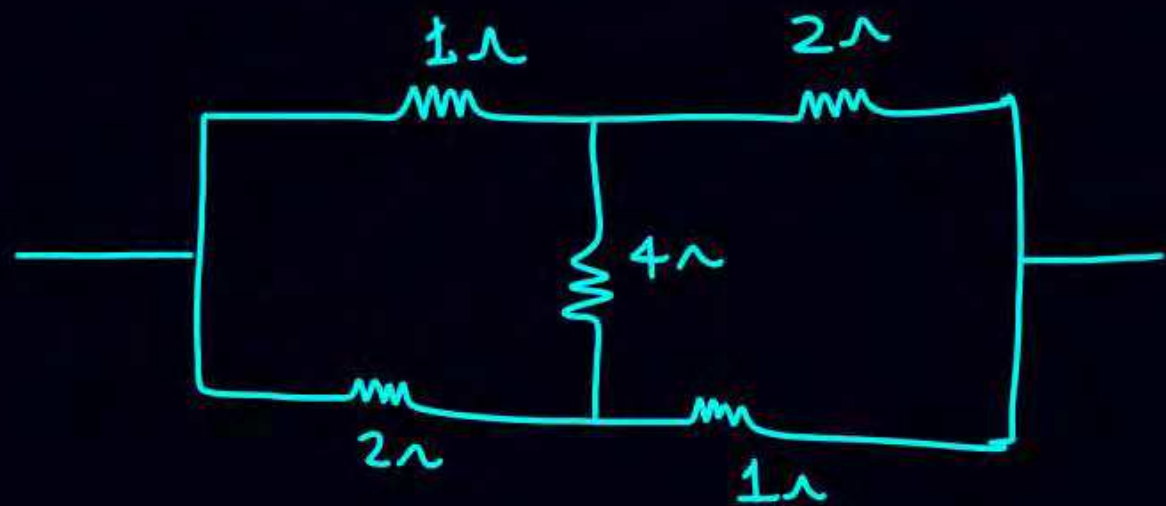

ATDB.uno

QUESTION -




In the circuit shown in the figure, the total charge is $750\text{ }\mu\text{C}$ and the voltage across capacitor C_2 is 20 V . Then the charge on capacitor C_2 is:

[JEE Mains-2020]

- 1 $590\text{ }\mu\text{C}$
- 2 $450\text{ }\mu\text{C}$
- 3 $650\text{ }\mu\text{C}$
- 4 $160\text{ }\mu\text{C}$

ATDB.uno

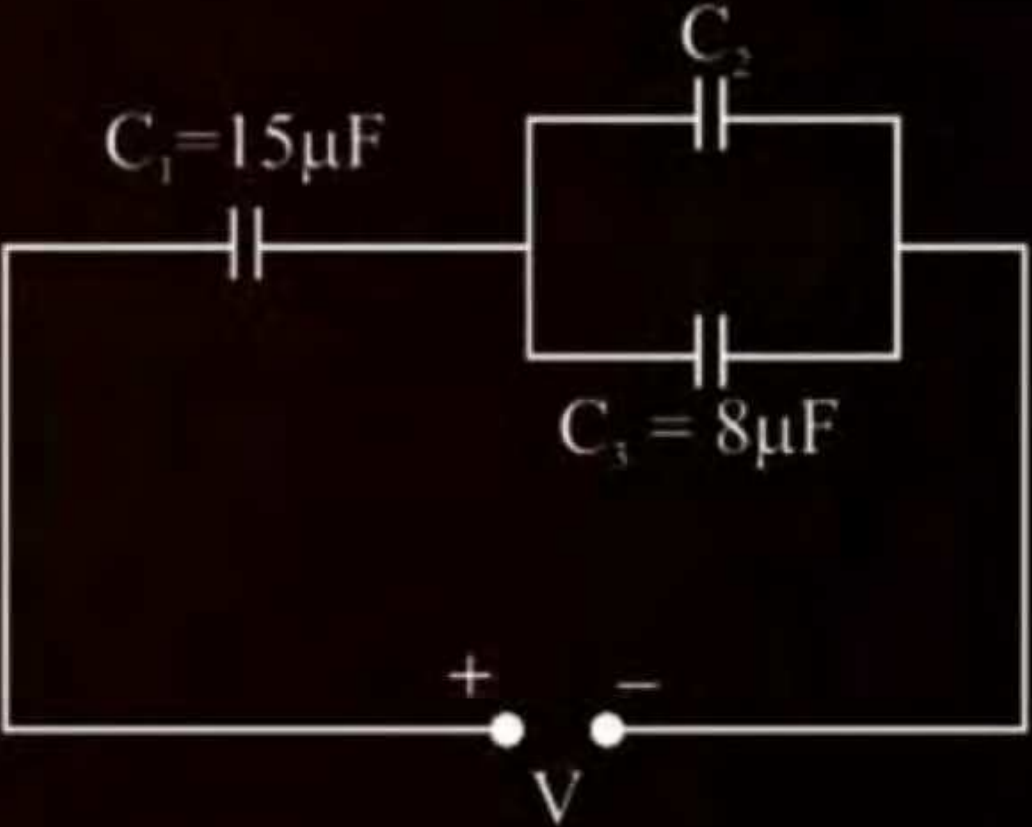

Ans. (1)

QUESTION –




In the circuit shown, charge on the $5\mu\text{F}$ capacitor is:

[JEE Mains-2020]

- 1 $5.45\mu\text{ C}$
- 2 $16.36\mu\text{ C}$
- 3 $10.90\mu\text{ C}$
- 4 $18.00\mu\text{ C}$

ATDB.uno

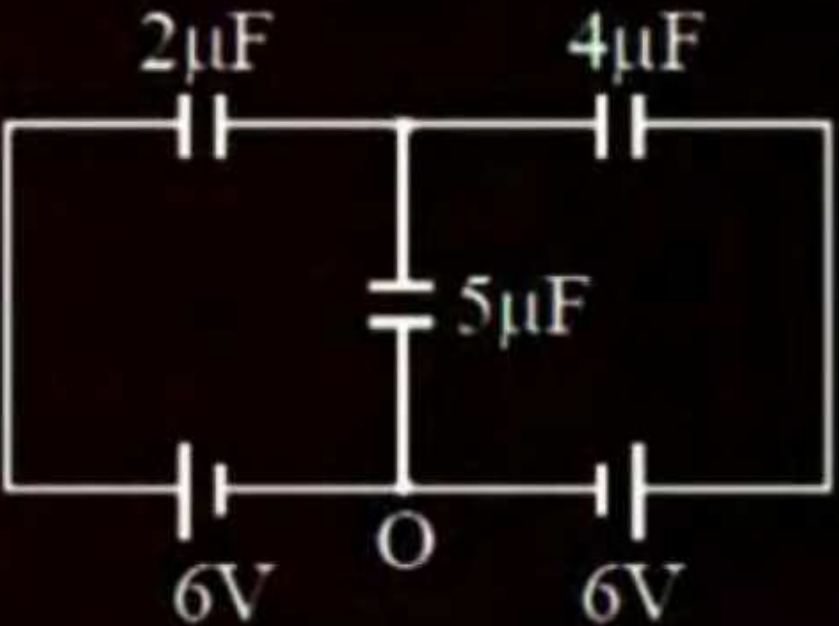

Ans. (2)


QUESTION -



Four identical rectangular plates with length, $l = 2\text{ cm}$ and breadth, $b = \frac{3}{2}\text{ cm}$ are arranged as shown in figure. The equivalent capacitance between A and C is $\frac{x\epsilon_0}{d}$. The value of x is _____. (Round off to the Nearest Integer)

[JEE Mains-2021]


ATDB.uno

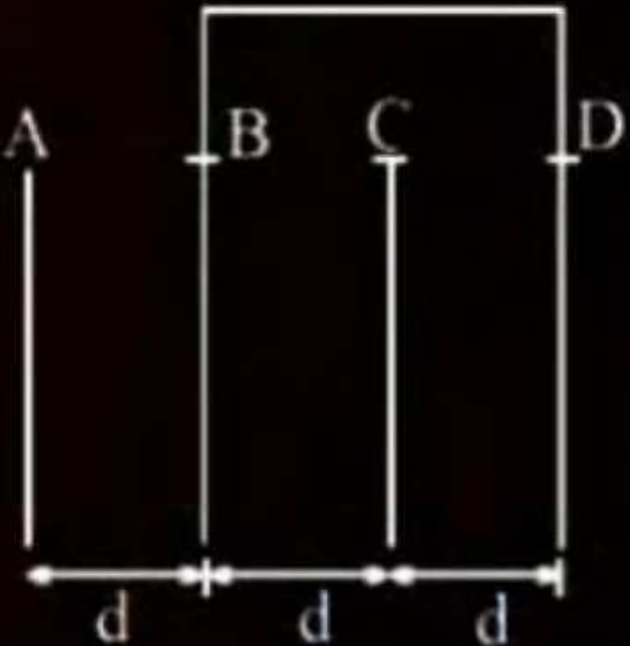

Ans. (2)

QUESTION –

A $2\ \mu\text{F}$ capacitor C_1 is first charged to a potential difference of $10\ \text{V}$ using a battery. Then the battery is removed and the capacitor is connected to an uncharged capacitor C_2 of $8\ \mu\text{F}$. The charge in C_2 on equilibrium condition is _____ μC . (Round off to the Nearest Integer)

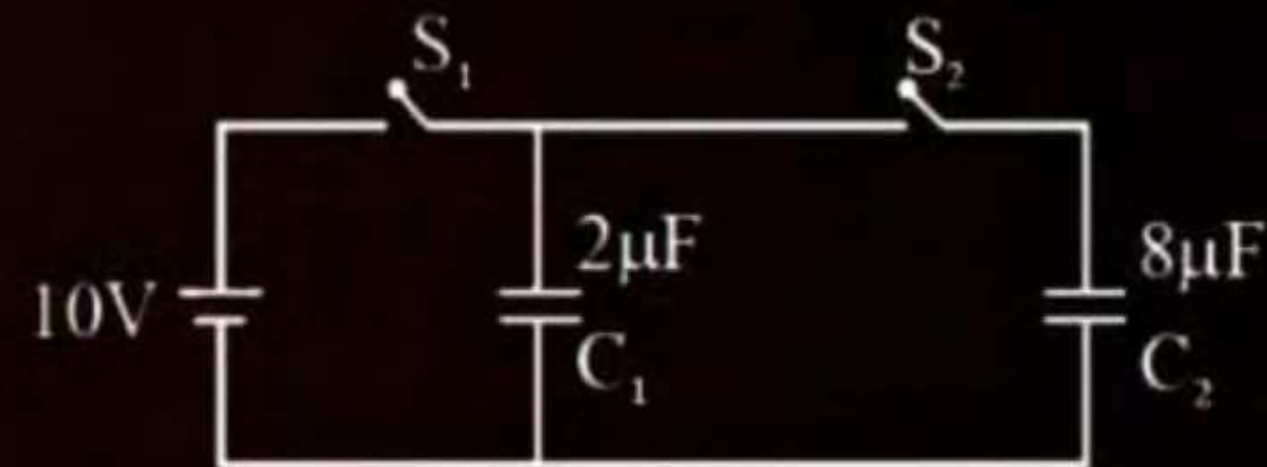
[JEE Mains-2021]**ATDB.uno****Ans. (16)**

QUESTION -



The equivalent capacitance between points A and B on below shown figure will be _____ μ F

[JEE Mains-2022]

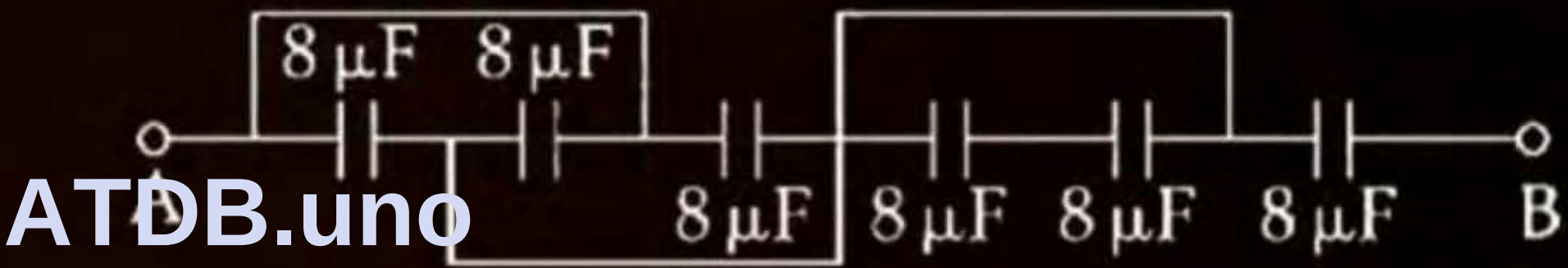


Ans. (6)

QUESTION -)



As shown in the figure, two parallel plate capacitors having equal plate area of 200 cm^2 are joined in such a way that $a \neq b$. The equivalent capacitance of the combination is $x\epsilon_0\text{ F}$. The value of x is _____.
[06 April 2023 - Shift 2]

ATDB.uno

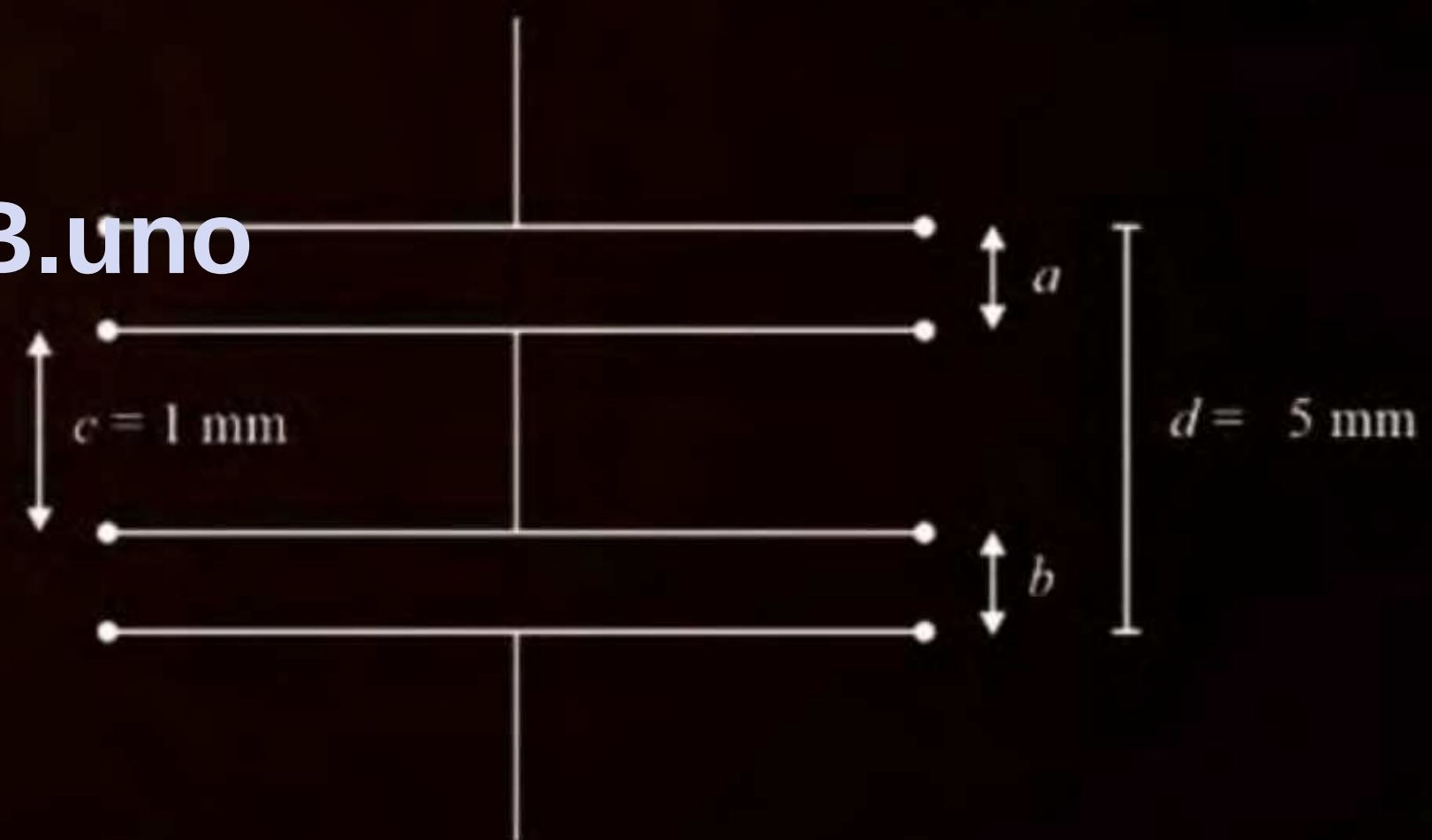

Ans : (5)

QUESTION -




The equivalent capacitance of the combination shown is

[10 April 2023 - Shift 1]

- 1 $2C$
- 2 $\frac{5}{3}C$
- 3 $\frac{C}{2}$
- 4 $4C$

ATDB.uno

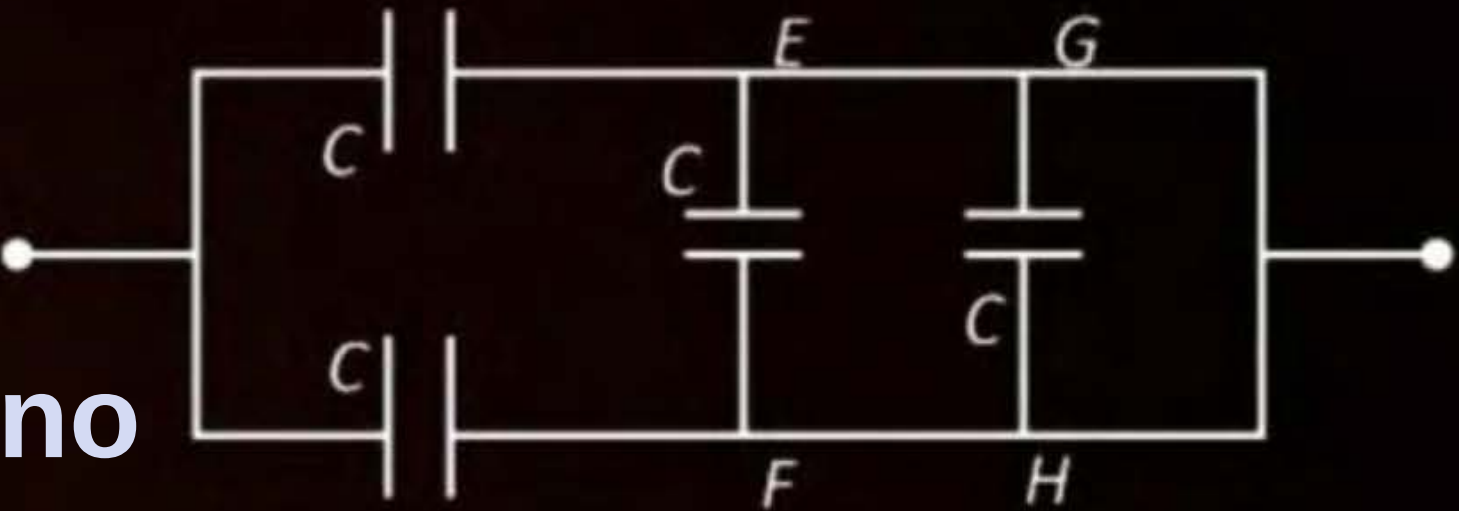


Ans. (1)

QUESTION -



In the given circuit. $C_1 = 2\mu\text{F}$, $C_2 = 0.2\mu\text{F}$, $C_3 = 2\mu\text{F}$, $C_4 = 4\mu\text{F}$, $C_5 = 2\mu\text{F}$, $C_6 = 2\mu\text{F}$. The charge stored on capacitor C_4 is _____ μC .
[11 April 2023 - Shift 2]

ATDB.uno

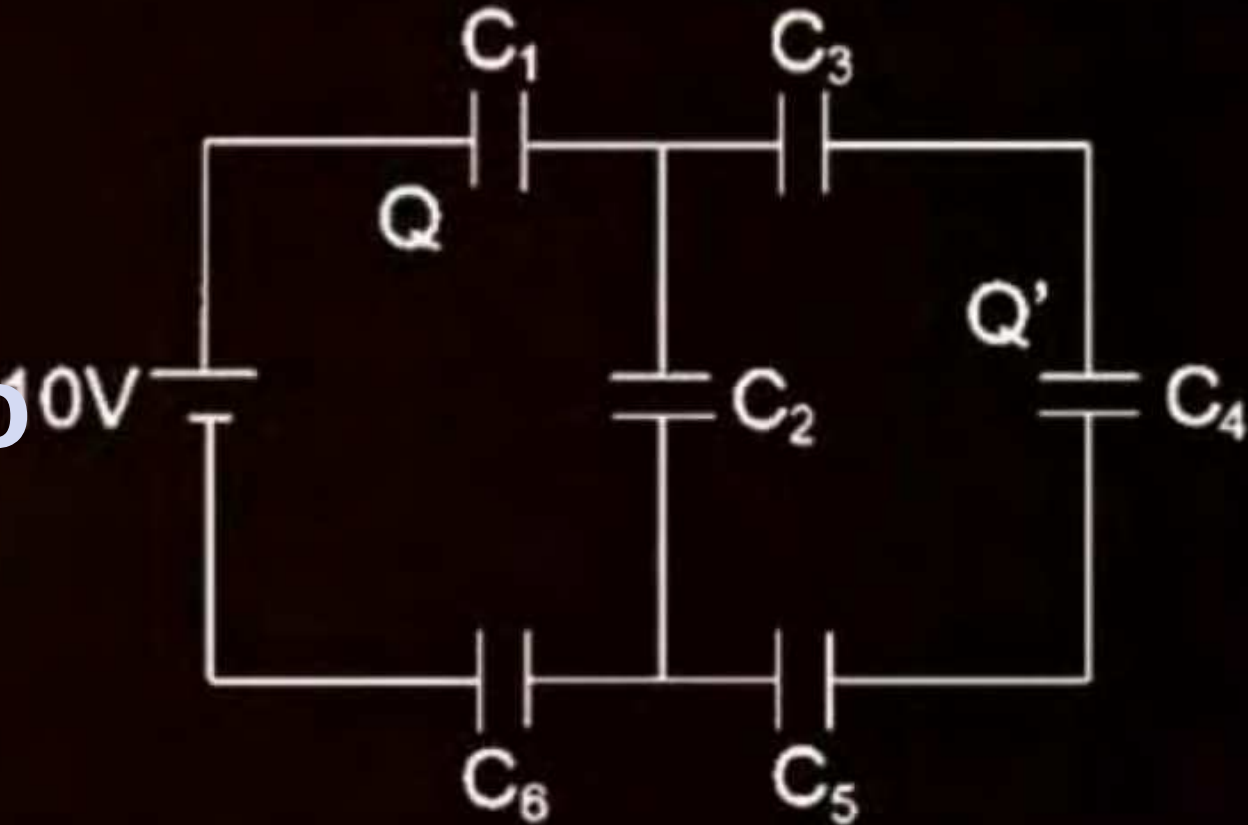

Ans. (4)


QUESTION -



In the given figure the total charge stored in the combination of capacitors is $100\mu\text{C}$.
 The value of 'x' is _____.

[15 April 2023 - Shift 1]

ATDB.uno

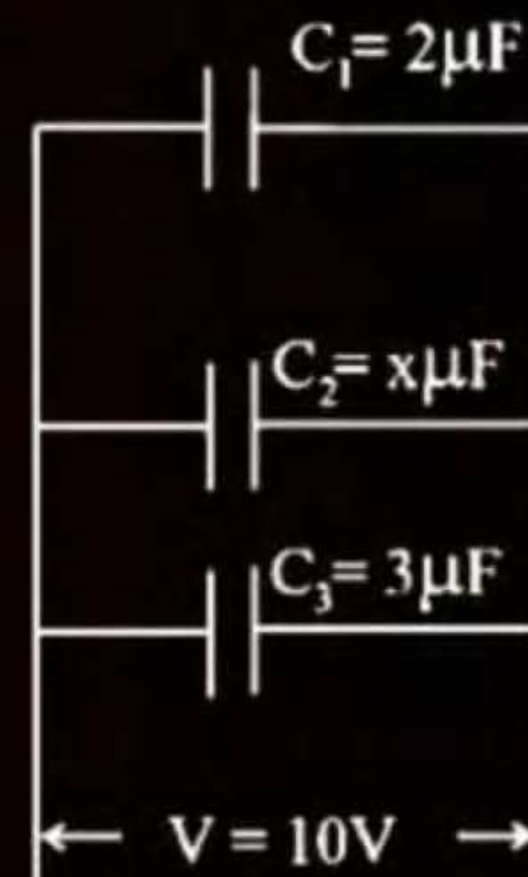


Ans. (5)

QUESTION -



The equivalent capacitance between points A and B on below shown figure will be _____ μ F

[JEE Mains-2022]

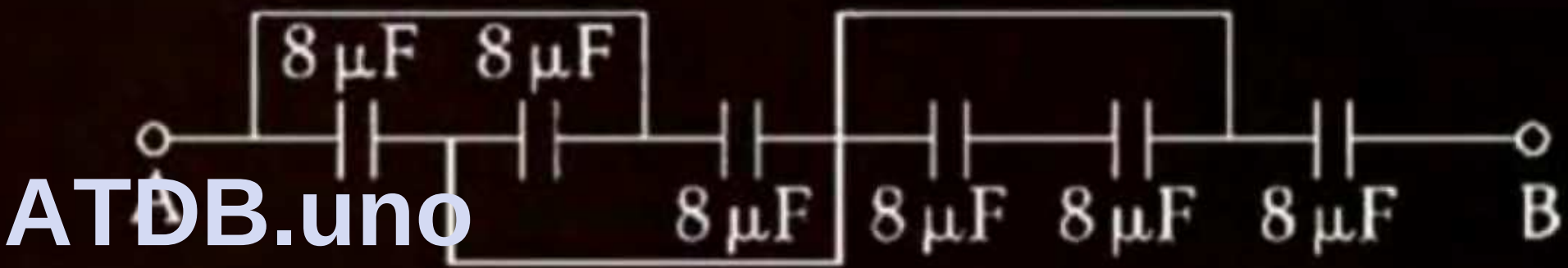


Ans. (6)

QUESTION

ε



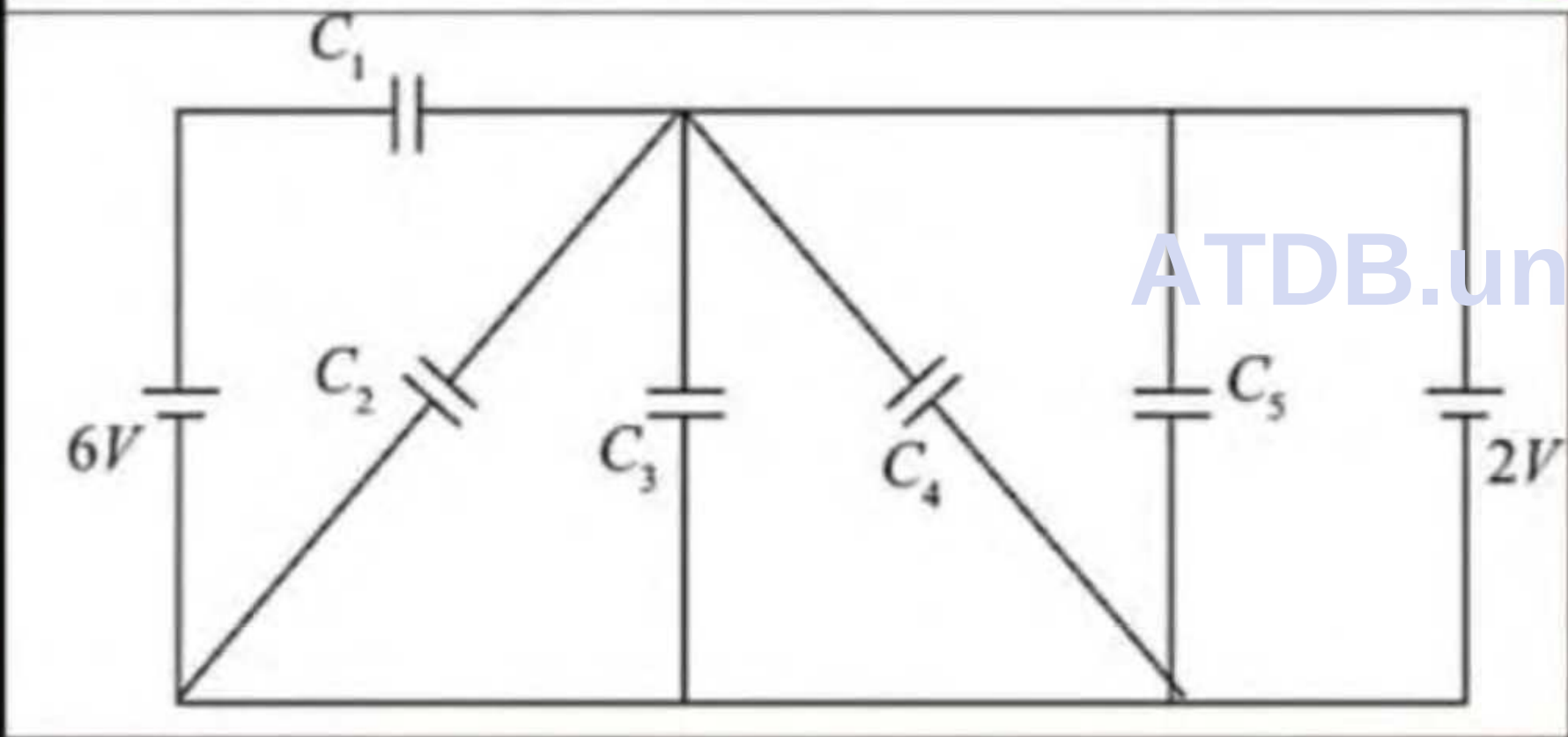12. In the following circuit $C_1 = 12\mu\text{F}$, $C_2 = C_3 = 4\mu\text{F}$ and $C_4 = C_5 = 2\mu\text{F}$. The charge stored in C_3 is _____ μC .
(JEE Adv. 2022)




Ans. (8)

QUESTION

$C_1 = \frac{A\epsilon_0}{d}$



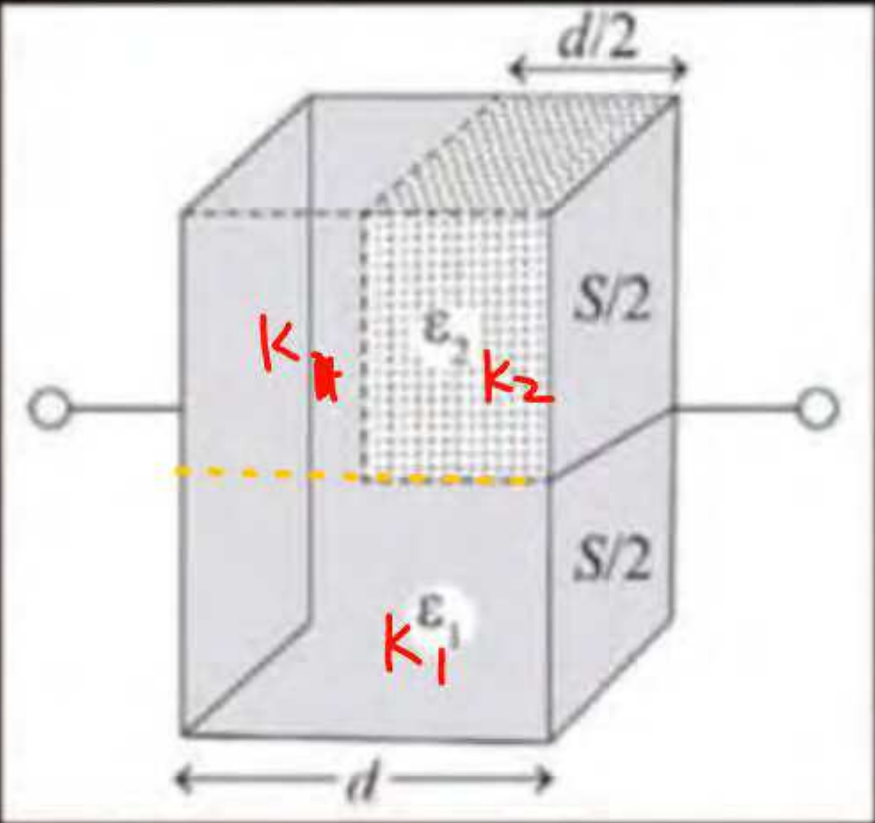14. A parallel plate capacitor having plates of area S and plate separation d , has capacitance C_1 in air. When two dielectrics of different relative permittivity's ($\epsilon_1 = 12$ and $\epsilon_2 = 4$) are introduced between the two plates as shown in the figure, the capacitance becomes C_2 . The ratio $\frac{C_2}{C_1}$ is (JEE Adv. 2015)



(1) $\frac{6}{5}$

(2) $\frac{5}{3}$

(3) $\frac{7}{5}$

(4) $\frac{7}{3}$


ATDB.uno



Ans. (4)

QUESTION

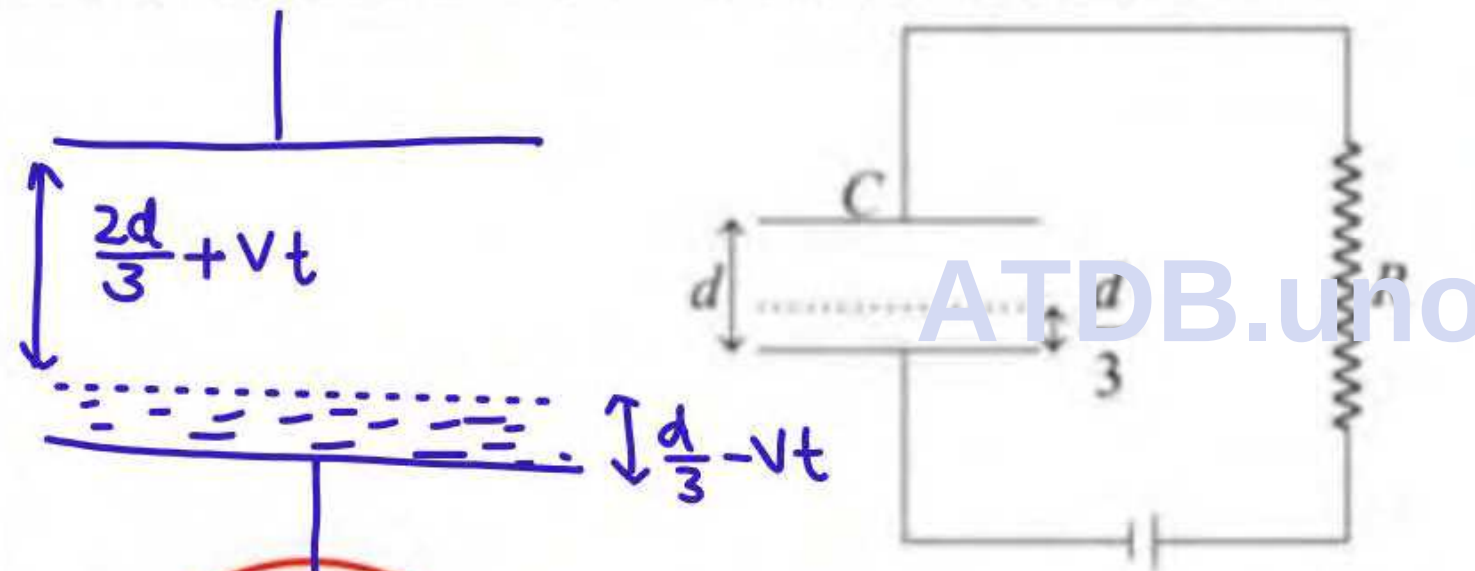26. A parallel plate capacitor C with plates of unit area and separation d is filled with a liquid of dielectric constant $K = 2$. The level of liquid is $d/3$ initially. Suppose the liquid level decreases at a constant speed v , the time constant as a function of time t is (IIT-JEE 2008)



$$\tau = RC_{eq}$$

- (a) $\frac{6\epsilon_0 R}{5d + 3vt}$
- (b) $\frac{(15d + 9vt)\epsilon_0 R}{2d^2 - 3dvt - 9v^2 t^2}$
- (c) $\frac{6\epsilon_0 R}{5d - 3vt}$
- (d) $\frac{(15d - 9vt)\epsilon_0 R}{2d^2 + 3dvt - 9v^2 t^2}$

QUESTION – 02




In the circuit shown, charge on the $5\mu\text{F}$ capacitor is:

[JEE Mains-2020]

- 1 $5.45\mu\text{ C}$
- 2 $16.36\mu\text{ C}$
- 3 $10.90\mu\text{ C}$
- 4 $18.00\mu\text{ C}$

ATDB.uno

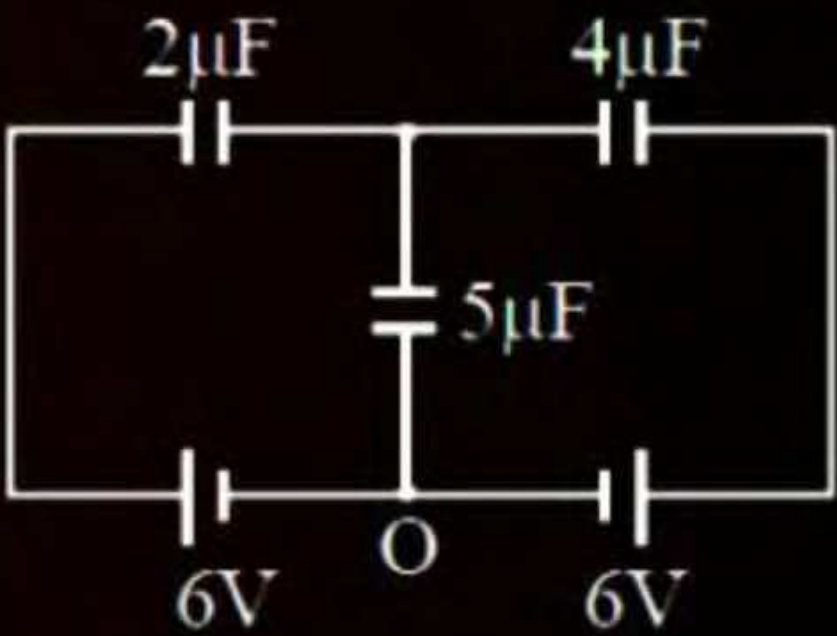

Ans. (2)

QUESTION – 03

Two equal capacitors are first connected in series and then in parallel. The ratio of the equivalent capacities in the two cases will be:

[JEE Mains-2021]

1 4 : 1

2 2 : 1

3 1 : 4

4 1 : 2

ATDB.uno

Ans. (3)

QUESTION – 04



Consider the combination of 2 capacitors C_1 and C_2 , with $C_2 > C_1$, when connected in parallel, the equivalent capacitance is $\frac{15}{4}$ time the equivalent capacitance of the same connected in series. Calculate the ratio of capacitors, $\frac{C_2}{C_1}$.

[JEE Mains-2021]

- 1 $\frac{15}{11}$
- 2 $\frac{111}{80}$
- 3 $\frac{29}{15}$
- 4 None of these

ATDB.uno

Ans. (4)


QUESTION – 07



Four identical rectangular plates with length, $l = 2\text{ cm}$ and breadth, $b = \frac{3}{2}\text{ cm}$ are arranged as shown in figure. The equivalent capacitance between A and C is $\frac{x\epsilon_0}{d}$. The value of x is _____. (Round off to the Nearest Integer)

[JEE Mains-2021]

ATDB.uno

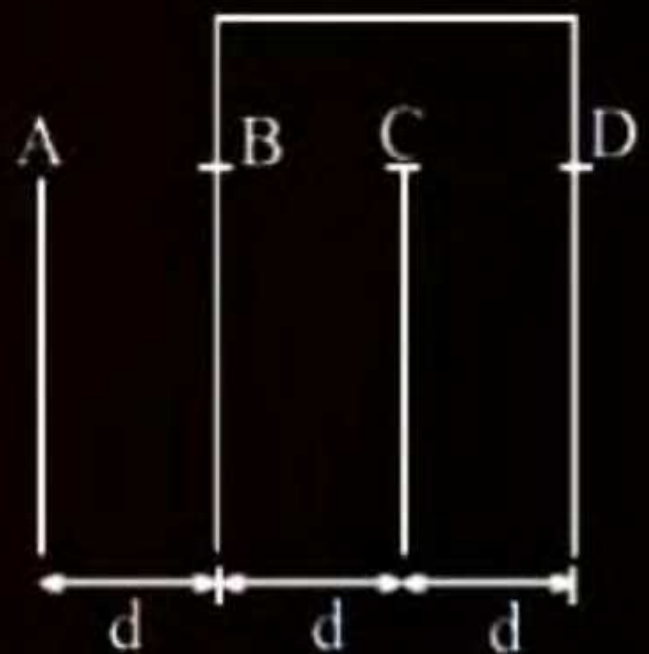


Ans. (2)

QUESTION – 08

A $2\ \mu\text{F}$ capacitor C_1 is first charged to a potential difference of $10\ \text{V}$ using a battery. Then the battery is removed and the capacitor is connected to an uncharged capacitor C_2 of $8\ \mu\text{F}$. The charge in C_2 on equilibrium condition is _____ μC . (Round off to the Nearest Integer)

[JEE Mains-2021]

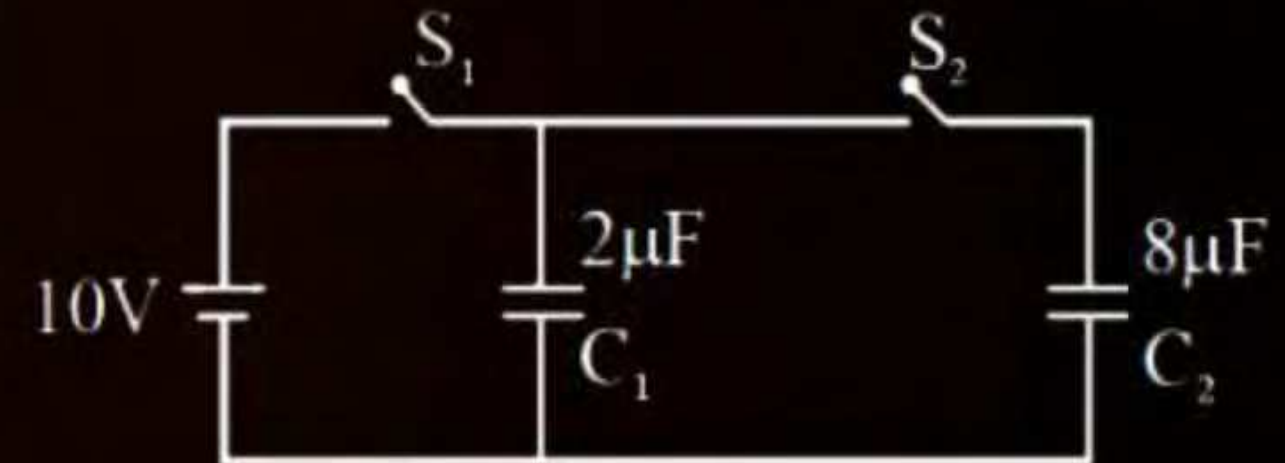ATDB.uno**Ans. (16)**


QUESTION – 12



Three capacitors $C_1 = 2\text{ }\mu\text{F}$, $C_2 = 6\text{ }\mu\text{F}$ and $C_3 = 12\text{ }\mu\text{F}$ are connected as shown in figure. Find the ratio of the charges on capacitors C_1 , C_2 and C_3 respectively: **[JEE Mains-2021]**

- 12 : 1 : 1
- 23 : 3 : 3
- 31 : 2 : 2
- 43 : 4 : 4

ATDB.uno

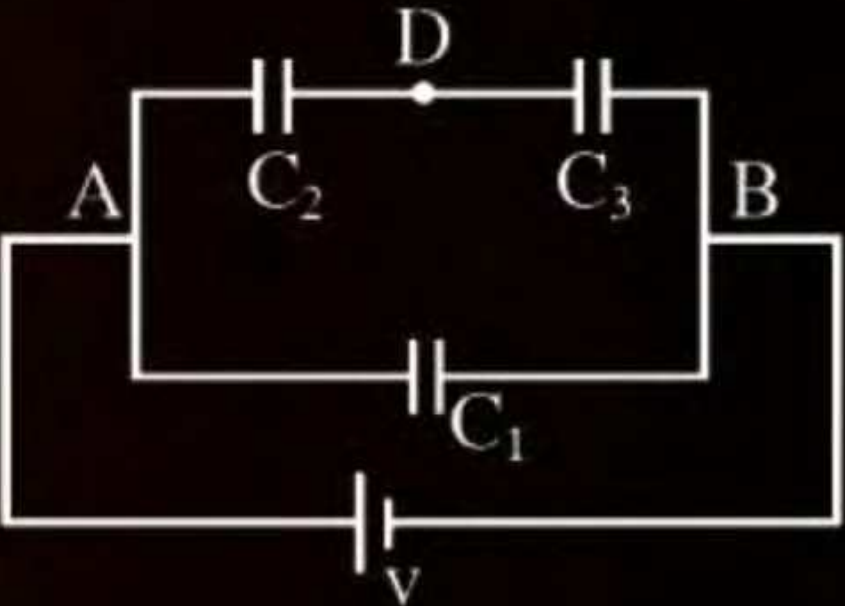

Ans. (3)

QUESTION – 15

The total charge on the system of capacitance $C_1 = 1\mu\text{F}$, $C_2 = 2\mu\text{F}$, $C_3 = 4\mu\text{F}$ and $C_4 = 3\mu\text{F}$ connected in parallel is (Assume a battery of 20V is connected to the combination)

[JEE Mains-2022]

1 $200\mu\text{C}$

2 200C

3 $10\mu\text{C}$

4 10C

ATDB.uno

Ans. (1)

QUESTION – 19

If the charge on a capacitor is increased by $2C$, the energy stored in increases by 44%.
The original charge on the capacitor is (in C): **[JEE Mains-2022]**

1 10

2 20

3 30

4 40

ATDB.uno

Ans. (1)

QUESTION – 20



The equivalent capacitance between points A and B on below shown figure will be _____ μ F

[JEE Mains-2022]



Ans. (6)

QUESTION – 21

Two metallic plates form a parallel plate capacitor. The distance between the plates is 'd'. A metal sheet of thickness $\frac{d}{2}$ and of area equal to area of each plate is introduced between the plates. What will be the ratio of the new capacitance to the original capacitance of the capacitor?

[JEE Mains-2022]

1 2 : 1

2 1 : 3

3 1 : 4

4 4 : 1

ATDB.uno

Ans. (1)

QUESTION – 22




The charge on capacitor of capacitance $15\mu\text{F}$ in the figure given below is :

[JEE Mains-2022]

- 1 $60\mu\text{C}$
- 2 $130\mu\text{C}$
- 3 $260\mu\text{C}$
- 4 $585\mu\text{C}$

ATDB.uno

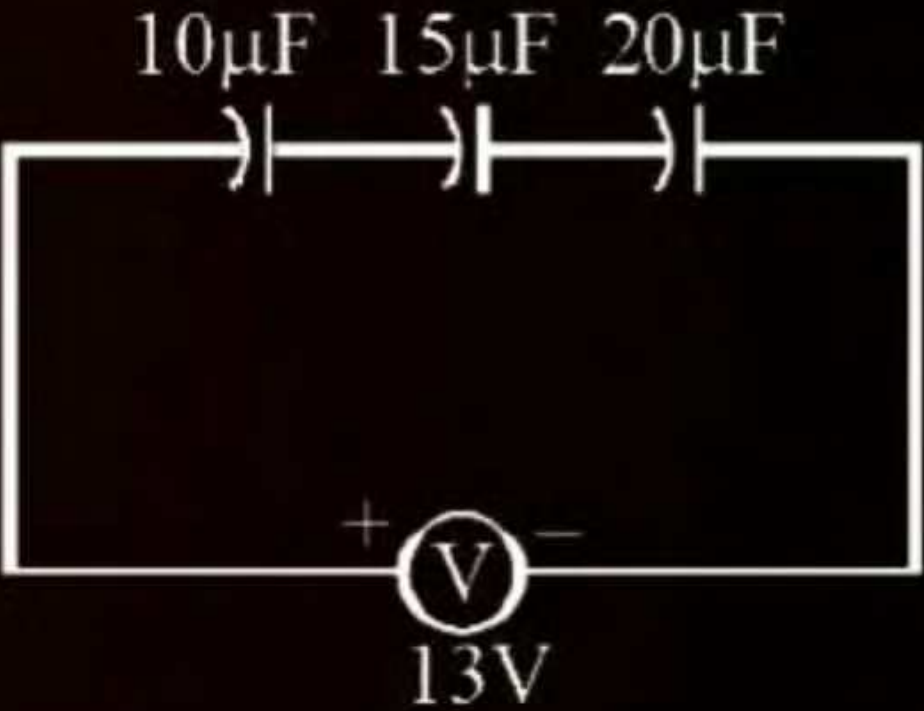

Ans. (1)

QUESTION – 23




A parallel plate capacitor with plate area A and plate separation $d = 2\text{ m}$ has a capacitance of $4\text{ }\mu\text{F}$. The new capacitance of the system if half of the space between them is filled with a dielectric material of dielectric constant $K = 3$ (as shown in figure) will be :

[JEE Mains-2022]

- 1 $2\mu\text{F}$
- 2 $32\mu\text{F}$
- 3 $6\mu\text{F}$
- 4 $8\mu\text{F}$

ATDB.uno

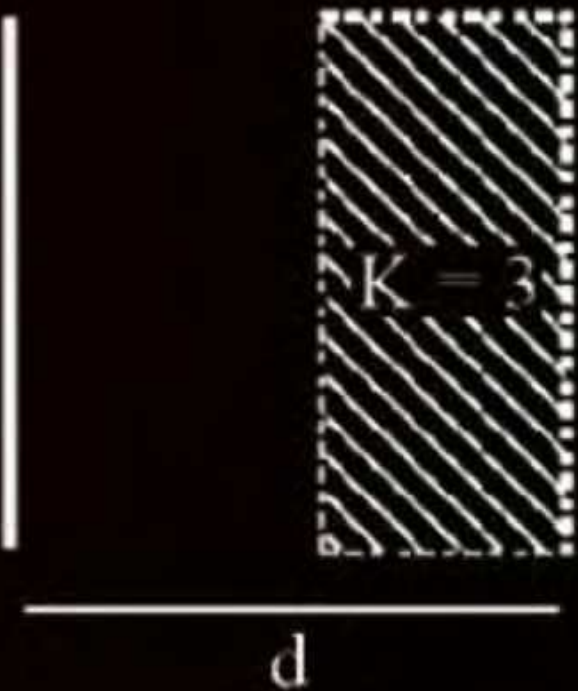

Ans. (3)

QUESTION – 24

A force of 10N acts on a charged particle placed between two plates of a charged capacitor. If one plate of capacitor is removed, then the force acting on that particle will be: **[JEE Mains-2022]**

- 1** 5 N
- 2** 10 N
- 3** 20 N
- 4** Zero

ATDB.uno

Ans. (1)

QUESTION – 25

A parallel plate capacitor filled with a medium of dielectric constant 10, is connected across a battery and is charged. The dielectric slab is replaced by another slab of dielectric constant 15. Then the energy of capacitor will: **[JEE Mains-2022]**

- 1** increase by 50%
- 2** decrease by 15%
- 3** increase by 25%
- 4** increase by 33%

ATDB.uno**Ans. (1)**

QUESTION – 40



In the reported figure, a capacitor is formed by placing a compound dielectric between the plates of parallel plate capacitor. The expression for the capacity of the said capacitor will be: (Given area of plate = A)

[JEE Mains-2021]

- 1


$\frac{15 K \epsilon_0 A}{34 d}$
- 2

$\frac{15 K \epsilon_0 A}{6 d}$
- 3

$\frac{25 K \epsilon_0 A}{6 d}$
- 4

$\frac{9 K \epsilon_0 A}{6 d}$

ATDB.uno

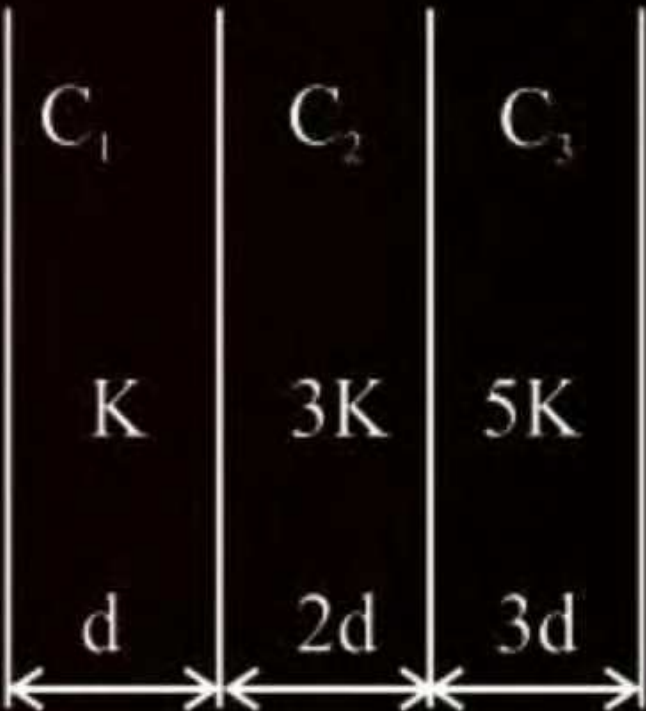

Ans. (1)

QUESTION – 49



A composite parallel plate capacitor is made up of two different dielectric materials with different thickness (t_1 and t_2) as shown in figure. The two different dielectric material are separated by a conducting foil F. The voltage of the conducting foil is _____V.

[JEE Mains-2022]

ATDB.uno



Ans. (60)

QUESTION – 59

A parallel plate capacitor with air between the plate has a capacitance of 15 pF. The separation between the plate becomes twice and the space between them is filled with a medium of dielectric constant 3.5. Then the capacitance becomes $\frac{x}{4}$ pF. The value of x is:

[24 January 2023 - Shift 2]

ATDB.uno

Ans. (105)

QUESTION – 60

A parallel plate capacitor has plate area 40cm^2 and plates separation 2 mm . The space between the plates is filled with a dielectric medium of a thickness 1 mm and dielectric constant 5 . The capacitance of the system is:

[25 January 2023 - Shift 1]

1 $24\epsilon_0\text{ F}$

2 $\frac{3}{10}\epsilon_0\text{ F}$

3 $\frac{10}{3}\epsilon_0\text{ F}$

4 $10\epsilon_0\text{ F}$

ATDB.uno

Ans. (3)

QUESTION – 61

A capacitor has capacitance $5\ \mu\text{F}$ when its parallel plates are separated by air medium of thickness d . A slab of material of dielectric constant 1.5 having area equal to that of plates but thickness $\frac{d}{2}$ is inserted between the plates. Capacitance of the capacitor in the presence of slab will be _____ μF .

[25 January 2023 - Shift 2]

ATDB.uno

Ans. (6)

QUESTION – 67




The equivalent capacitance of the combination shown is

[10 April 2023 - Shift 1]

- 1 $2C$
- 2 $\frac{5}{3}C$
- 3 $\frac{C}{2}$
- 4 $4C$

ATDB.uno

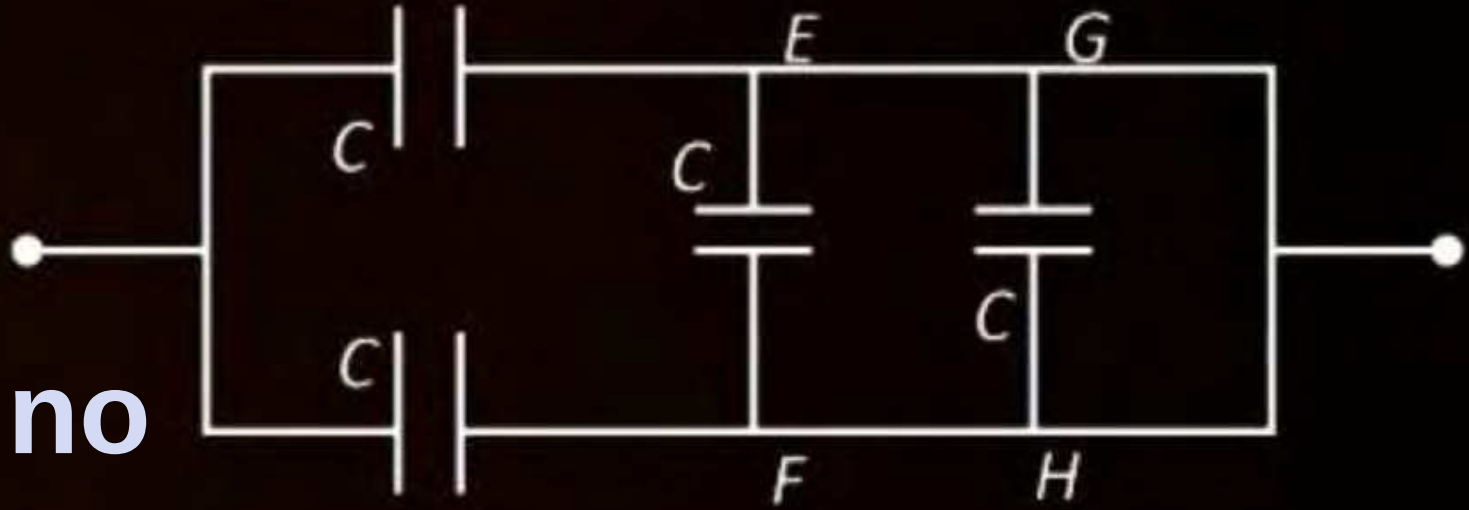

Ans. (1)

QUESTION – 68

The distance between two plates of a capacitor is d and its capacitance is C_1 , when air is the medium between the plates. If a metal sheet of thickness $\frac{2d}{3}$ and of the same area as plate is introduced between the plates, the capacitance of the capacitor becomes C_2 . The ratio $\frac{C_2}{C_1}$ is.

[10 April 2023 - Shift 2]

ATDB.uno

1 3 : 1

2 2 : 1

3 4 : 1

4 1 : 1

Ans. (1)

QUESTION – 71

A capacitor of capacitance C is charged to a potential V . The flux of the electric field through a closed surface enclosing the positive plate of the capacitor is:

[11 April 2023 - Shift 2]

- 1 $\frac{CV}{\epsilon_0}$
- 2 Zero
- 3 $\frac{2CV}{\epsilon_0}$
- 4 $\frac{CV}{2\epsilon_0}$


ATDB.uno

Ans. (1)

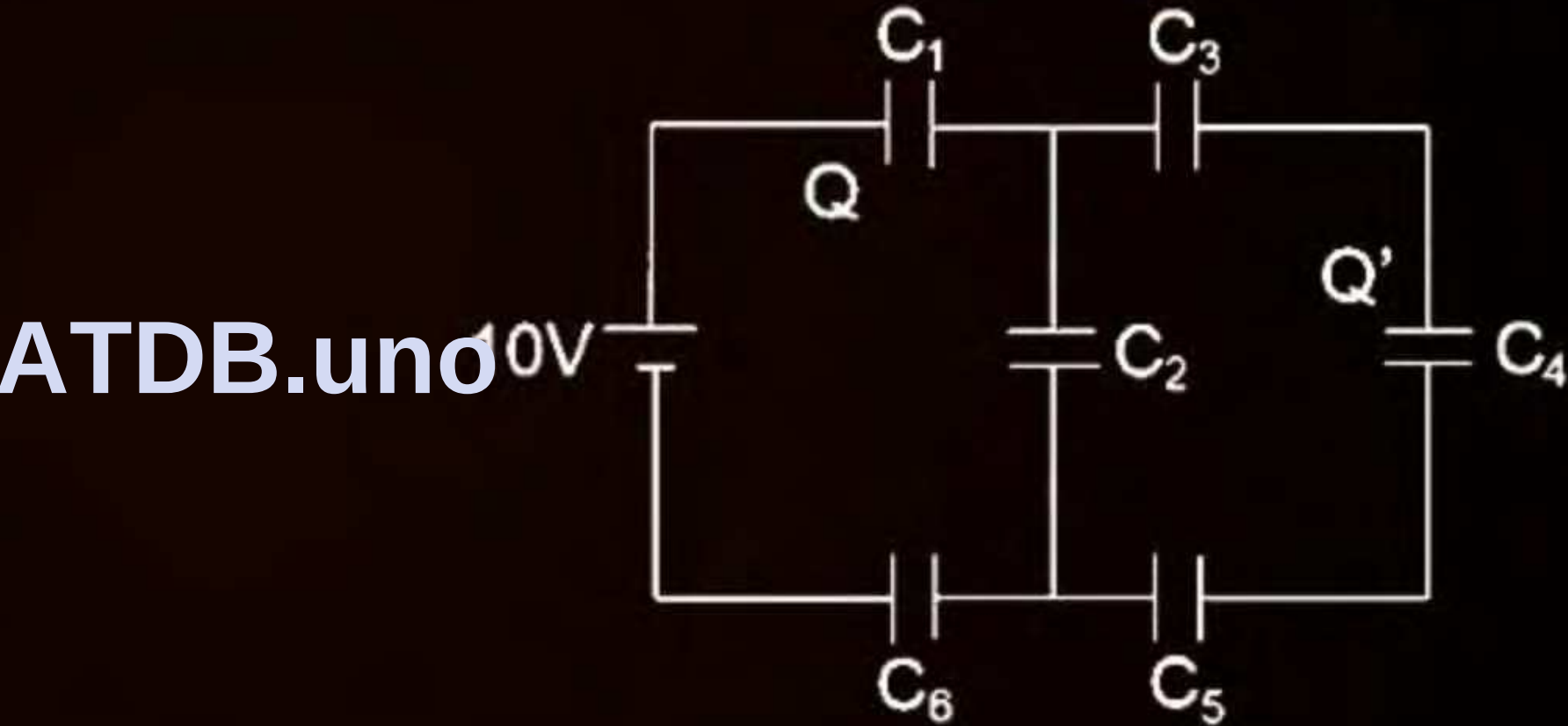QUESTION – 72




In the given circuit. $C_1 = 2\mu\text{F}$, $C_2 = 0.2\mu\text{F}$, $C_3 = 2\mu\text{F}$, $C_4 = 4\mu\text{F}$, $C_5 = 2\mu\text{F}$, $C_6 = 2\mu\text{F}$. The charge stored on capacitor C_4 is _____ μC .
[11 April 2023 - Shift 2]



Ans. (4)

QUESTION

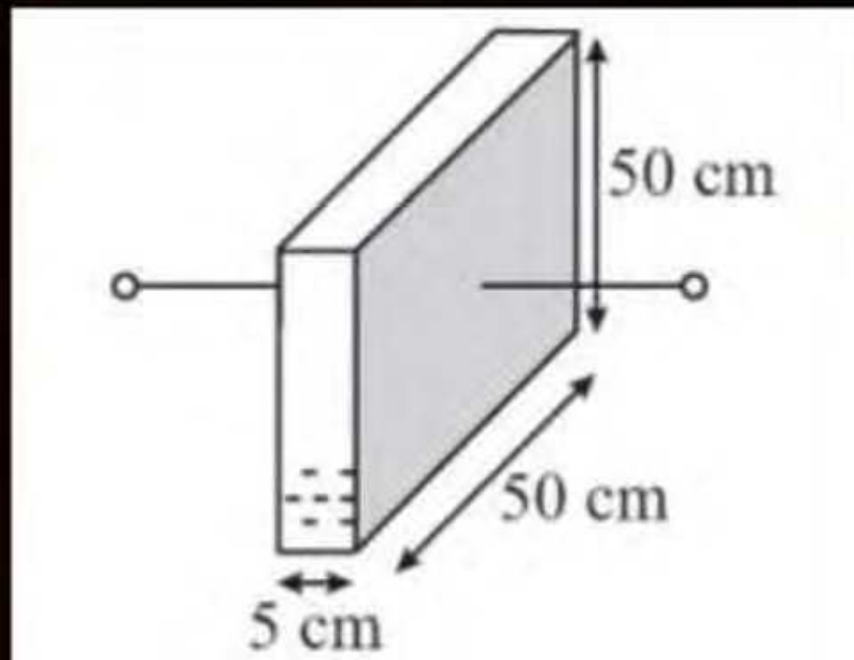8. A container has a base of $50 \text{ cm} \times 5 \text{ cm}$ and height 50 cm , as shown in the figure. It has two parallel electrically conducting walls each of area $50 \text{ cm} \times 50 \text{ cm}$. The remaining walls of the container are thin and non-conducting. The container is being filled with a liquid of dielectric constant 3 at a uniform rate of $250 \text{ cm}^3 \text{ s}^{-1}$. What is the value of the capacitance of the container after 10 seconds? [Given: Permittivity of free space $\epsilon_0 = 9 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$, the effects of the non-conducting walls on the capacitance are negligible] (JEE Adv. 2023)




- | | |
|---------------------|----------------------|
| (1) 27 pF | (2) 63 pF |
| (3) 81 pF | (4) 135 pF |

Ans. (2)

QUESTION



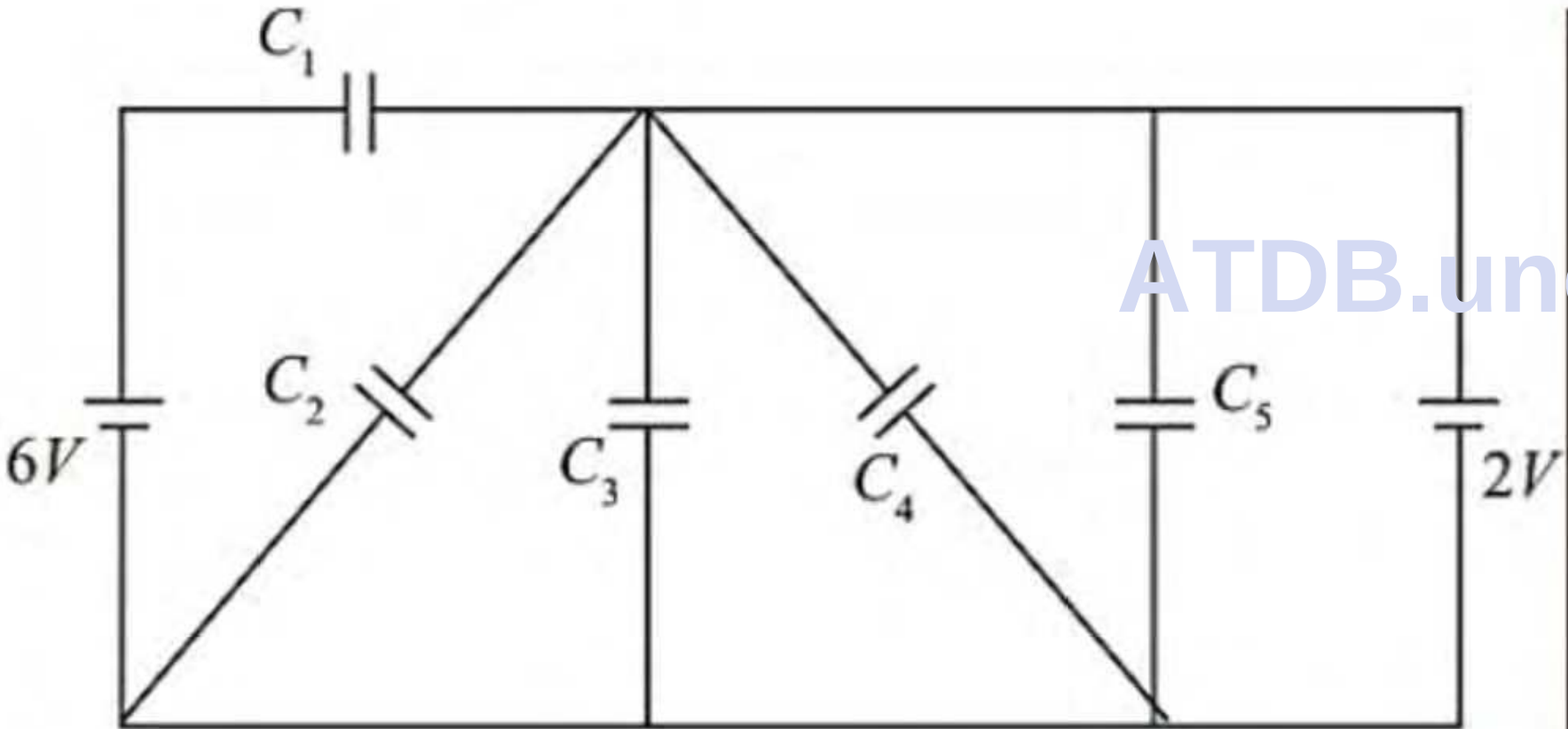12. In the following circuit $C_1 = 12\mu\text{F}$, $C_2 = C_3 = 4\mu\text{F}$ and $C_4 = C_5 = 2\mu\text{F}$. The charge stored in C_3 is _____ μC .
(JEE Adv. 2022)




Ans. (8)

QUESTION



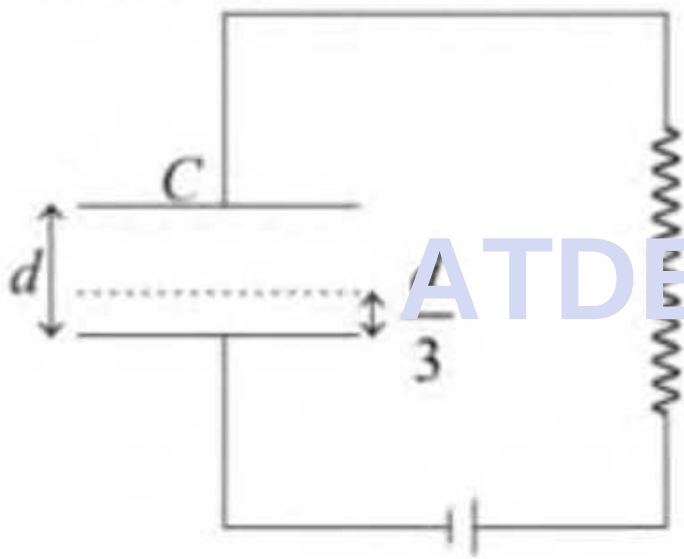26. A parallel plate capacitor C with plates of unit area and separation d is filled with a liquid of dielectric constant $K = 2$. The level of liquid is $d/3$ initially. Suppose the liquid level decreases at a constant speed v , the time constant as a function of time t is (IIT-JEE 2008)



- (a) $\frac{6\epsilon_0 R}{5d + 3vt}$

(c) $\frac{6\epsilon_0 R}{5d - 3vt}$
- (b) $\frac{(15d + 9vt)\epsilon_0 R}{2d^2 - 3dvt - 9v^2 t^2}$

(d) $\frac{(15d - 9vt)\epsilon_0 R}{2d^2 + 3dvt - 9v^2 t^2}$

Ans : (a)



HCV Ques

ATDB.uno




9. The negative plate of a parallel plate capacitor is given a charge of -20×10^{-8} C. Find the charges appearing on the four surfaces of the capacitor plates.

ATDB.uno

Ans. $Q = 10 \times 10^{-8}$ C.



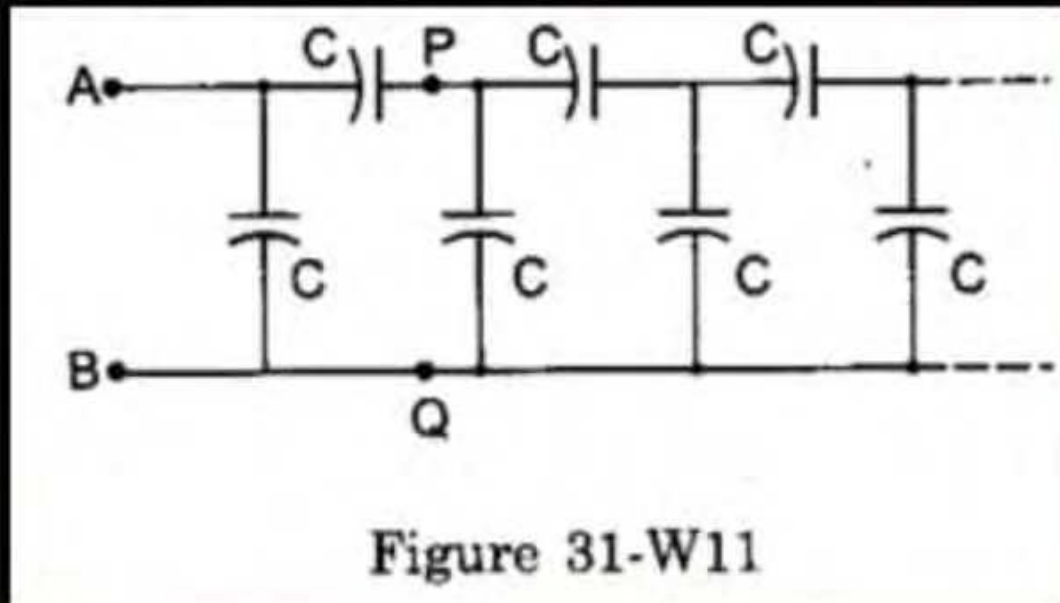13. Find the capacitance of the infinite ladder shown in figure (31-W11).



ATDB.uno

Ans. $C = \frac{C + \sqrt{C^2 + 4C^2}}{1} = \frac{1 + \sqrt{5}}{2} C$



14. Find the energy stored in the electric field produced by a metal sphere of radius R containing a charge Q .

ATDB.uno

Ans. $U = \frac{Q^2}{2C} = \frac{Q^2}{8\pi\epsilon_0 R}$




16. *An uncharged capacitor is connected to a battery. Show that half the energy supplied by the battery is lost as heat while charging the capacitor.*

ATDB.uno

Ans. $U = \frac{1}{2} CV^2 = \frac{1}{2} QV.$



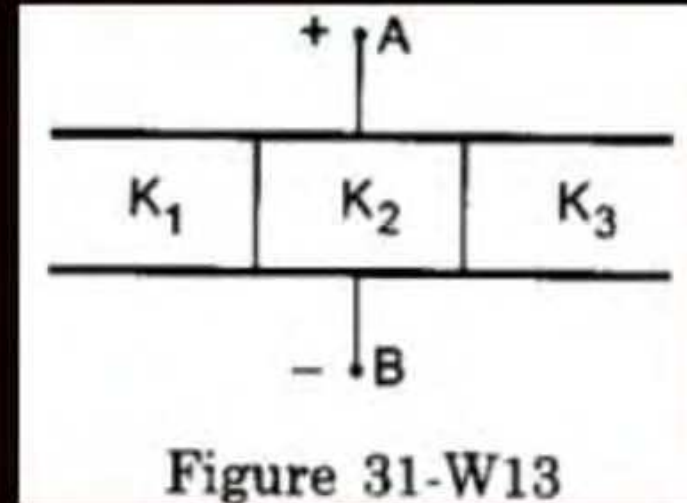19. The space between the plates of a parallel-plate capacitor of capacitance C is filled with three dielectric slabs of identical size as shown in figure (31-W13). If the dielectric constants of the three slabs are K_1 , K_2 and K_3 , find the new capacitance.



ATDB.uno

Ans. *

EXERCISES

1. When 1.0×10^{12} electrons are transferred from one conductor to another, a potential difference of 10 V appears between the conductors. Calculate the capacitance of the two-conductor system.

ATDB.uno

Ans. $1.6 \times 10^{-8} \text{ F}$



2. The plates of a parallel-plate capacitor are made of circular discs of radii 5.0 cm each. If the separation between the plates is 1.0 mm, what is the capacitance ?

ATDB.uno

Ans. $6.95 \times 10^{-5} \mu\text{F}$



4. A parallel-plate capacitor having plate area 25 cm^2 and separation 1.00 mm is connected to a battery of 6.0 V . Calculate the charge flown through the battery. How much work has been done by the battery during the process ?

ATDB.uno

Ans. $1.33 \times 10^{-10} \text{ C}$, $8.0 \times 10^{-10} \text{ J}$



6. Find the charges on the three capacitors connected to a battery as shown in figure (31-E1). Take $C_1 = 2.0 \mu\text{F}$, $C_2 = 4.0 \mu\text{F}$, $C_3 = 6.0 \mu\text{F}$ and $V = 12$ volts.

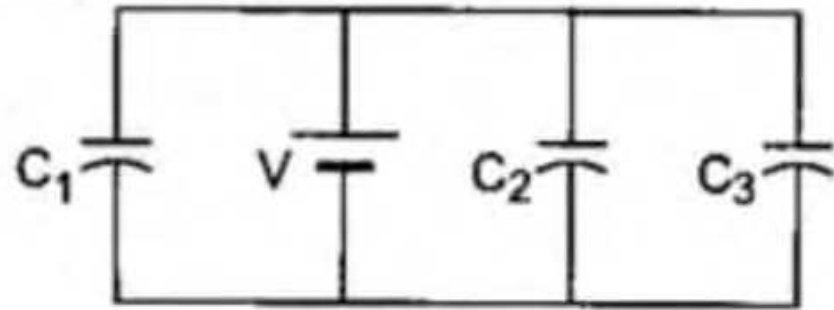


Figure 31-E1

ATDB.uno

Ans. $24 \mu\text{C}$, $48 \mu\text{C}$, $72 \mu\text{C}$



8. Find the charge appearing on each of the three capacitors shown in figure (31-E2).

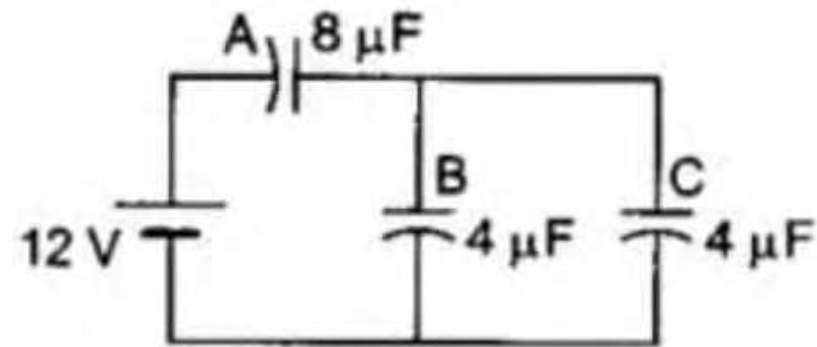


Figure 31-E2

ATDB.uno

Ans. $48\ \mu\text{C}$ on the $8\ \mu\text{F}$ capacitor and $24\ \mu\text{C}$ on each of the



9. Take $C_1 = 4.0 \mu\text{F}$ and $C_2 = 6.0 \mu\text{F}$ in figure (31-E3). Calculate the equivalent capacitance of the combination between the points indicated.

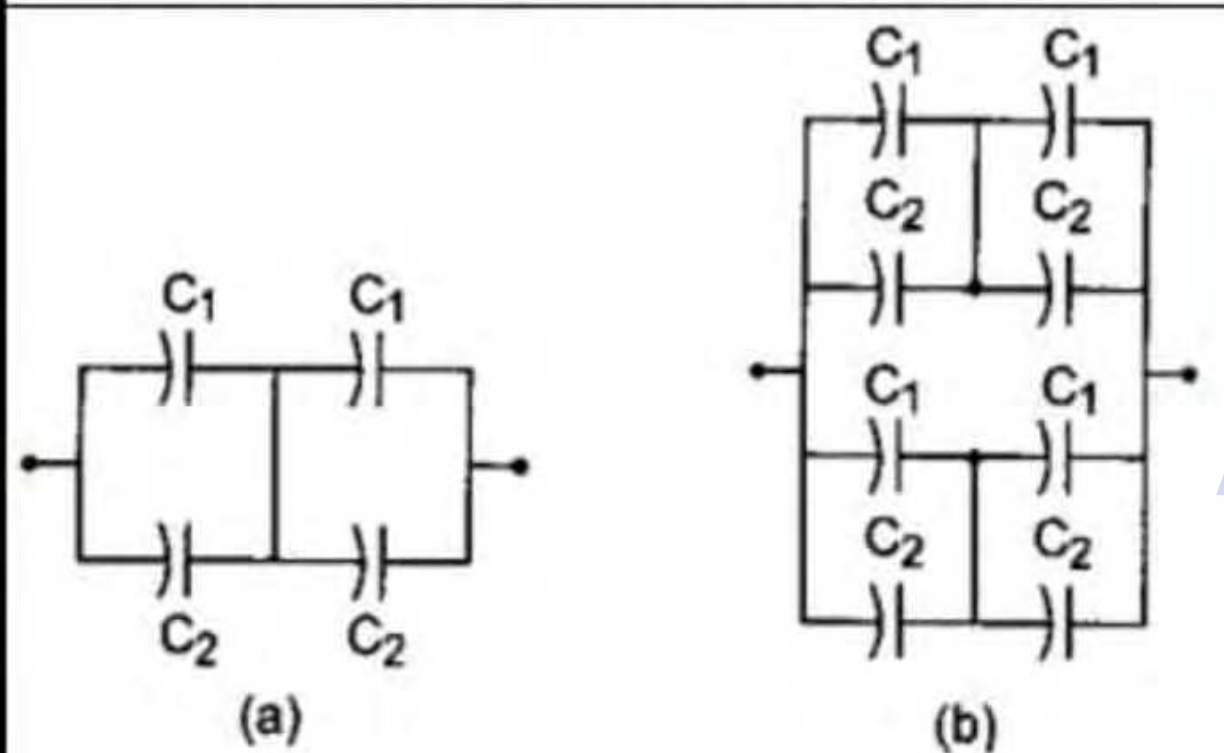


Figure 31-E3

ATDB.uno

Ans. (a) $5 \mu\text{F}$, (b) $10 \mu\text{F}$



10. Find the charge supplied by the battery in the arrangement shown in figure (31-E4).

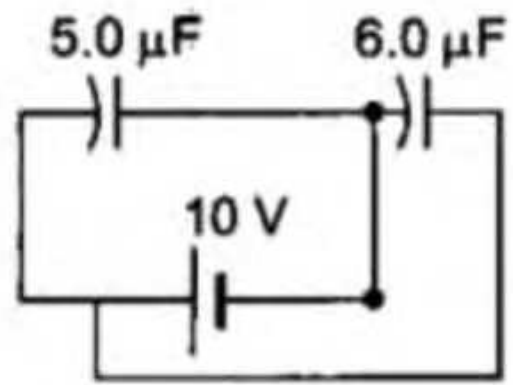


Figure 31-E4

ATDB.uno

Ans. $110\ \mu\text{C}$



16. Find the equivalent capacitance of the system shown in figure (31-E8) between the points *a* and *b*.

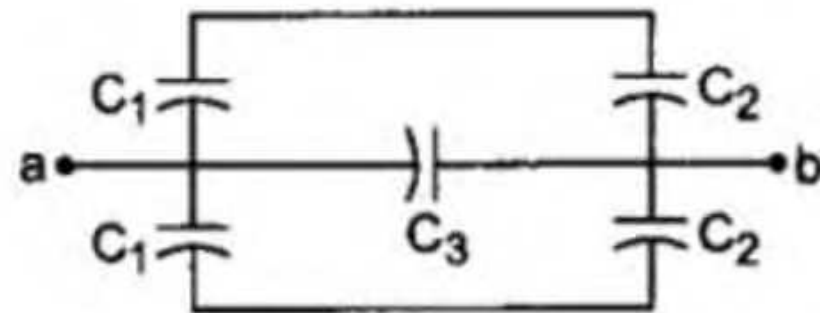


Figure 31-E8

ATDB.uno

Ans. $C_3 + \frac{2C_1C_2}{C_1 + C_2}$



20. Each capacitor shown in figure (31-E10) has a capacitance of $5.0 \mu\text{F}$. The emf of the battery is 50 V . How much charge will flow through AB if the switch S is closed ?

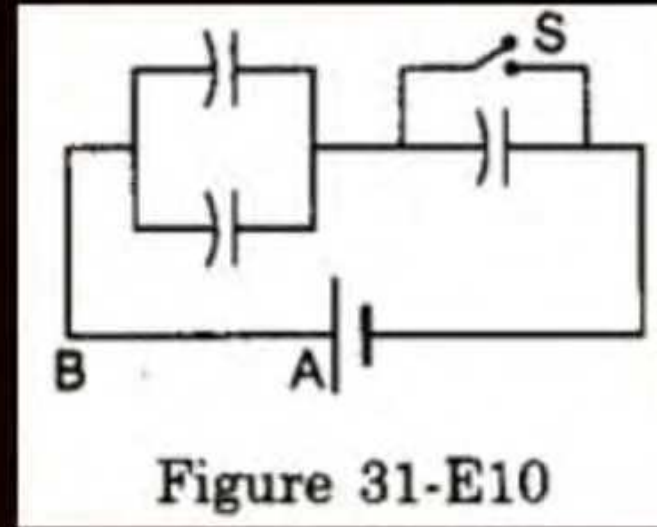





Figure 31-E10

ATDB.uno

Ans. $3.3 \times 10^{-4} \text{ C}$



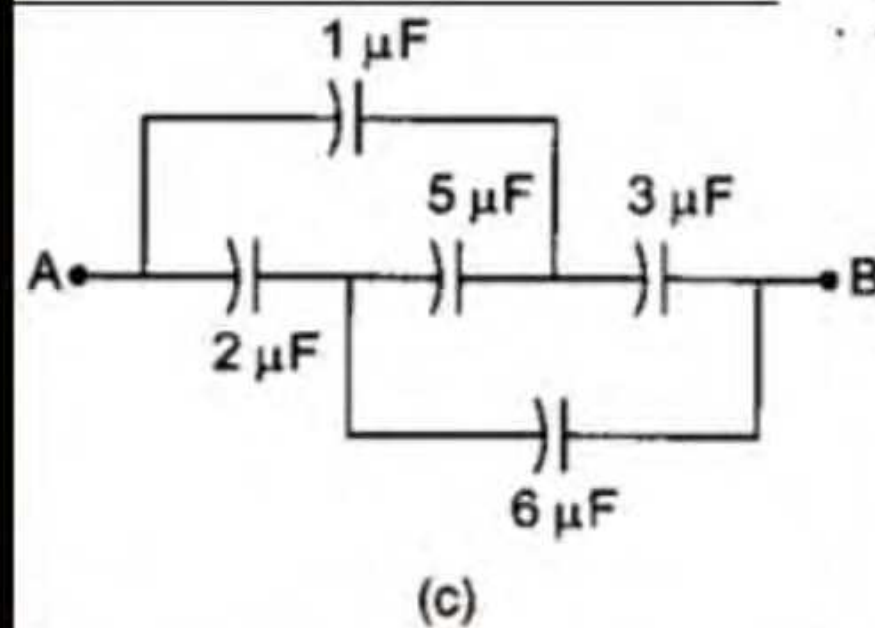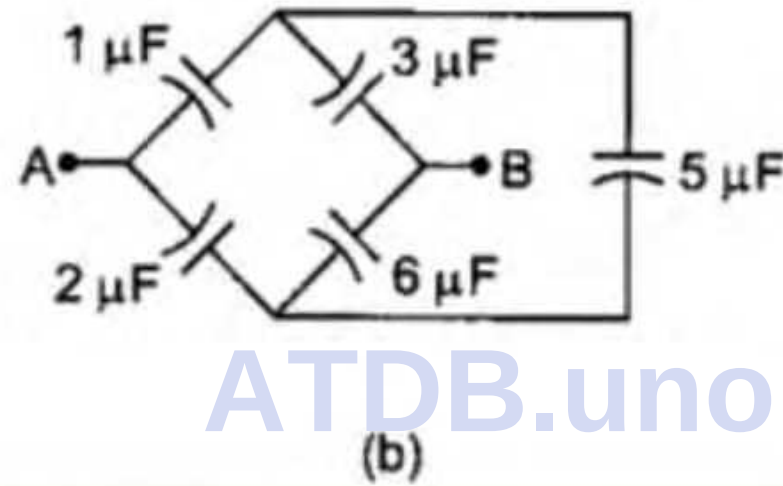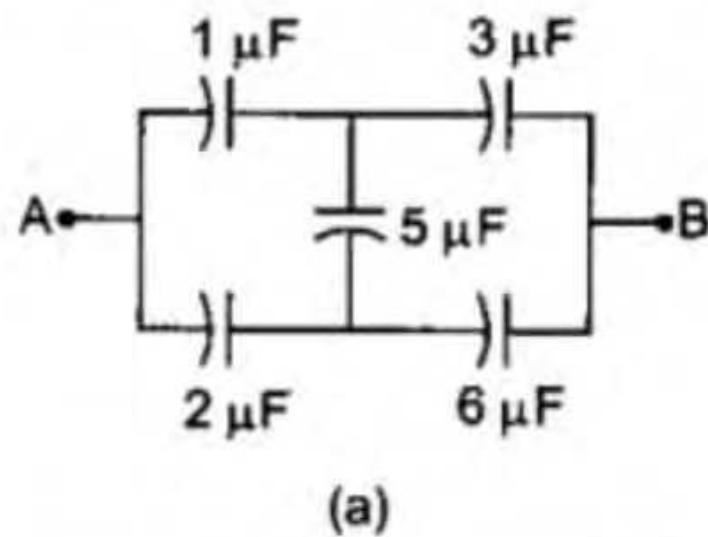24. Convince yourself that parts (a), (b) and (c) of figure (31-E13) are identical. Find the capacitance between the points *A* and *B* of the assembly.



Ans. $2.25 \mu\text{F}$



25. Find the potential difference $V_a - V_b$ between the points a and b shown in each part of the figure (31-E14).

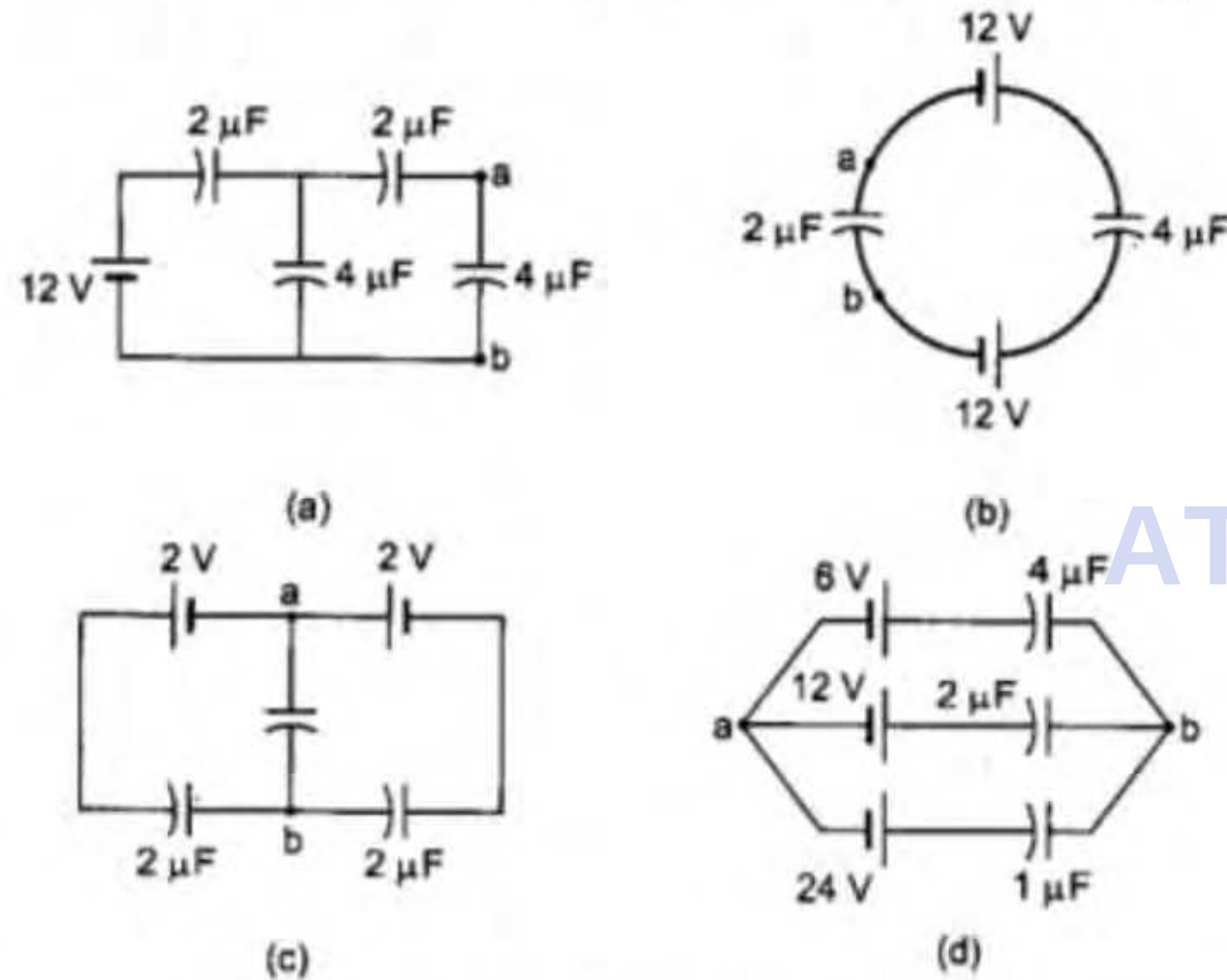


Figure 31-E14

Ans. (a) $\frac{12}{11}\text{ V}$ (b) -8 V (c) zero (d) -10.3 V



26. Find the equivalent capacitances of the combinations shown in figure (31-E15) between the indicated points.

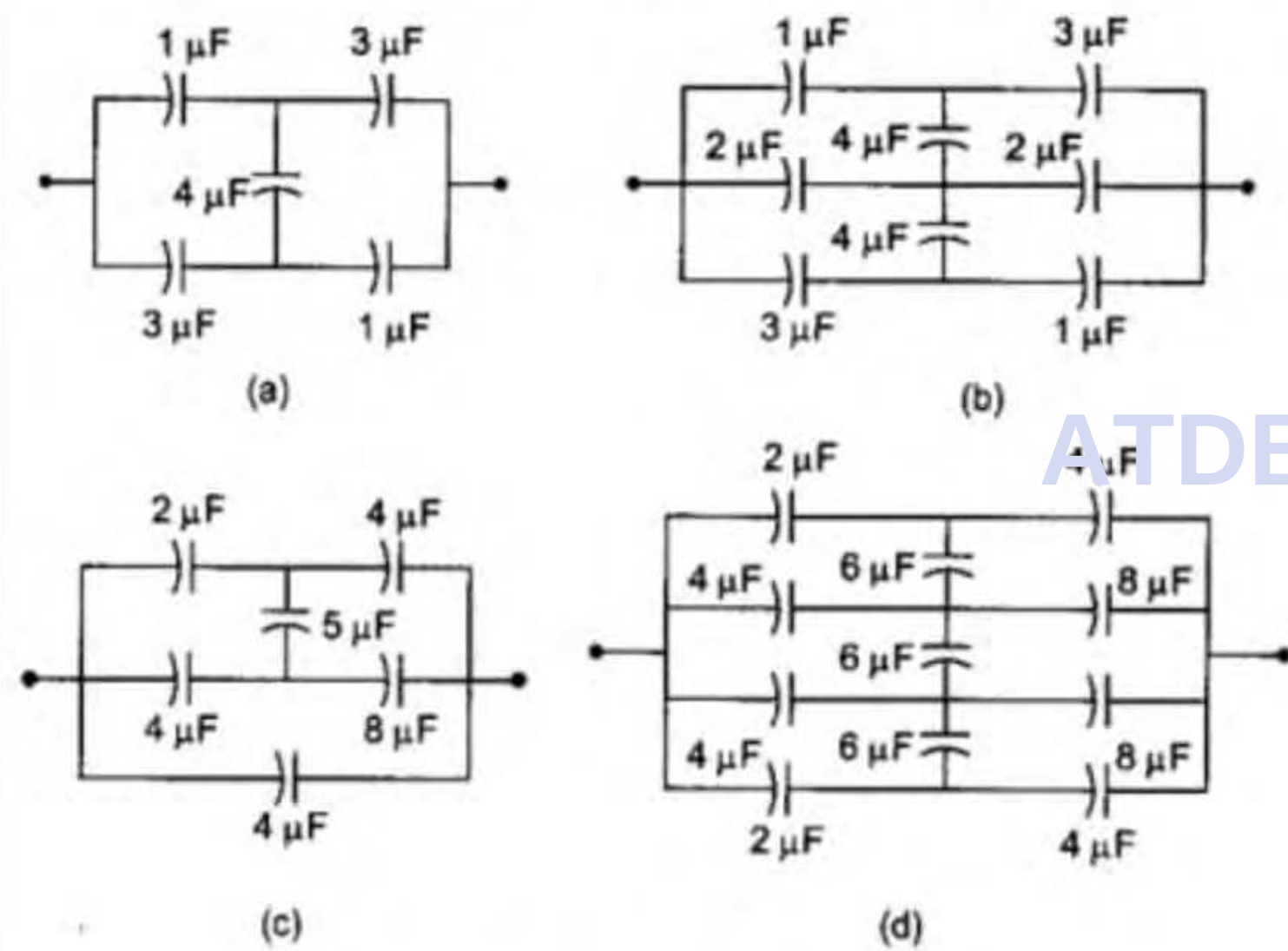


Figure 31-E15

Ans (a) $\frac{11}{2}\ \mu\text{F}$ (b) $\frac{11}{2}\ \mu\text{F}$ (c) $8\ \mu\text{F}$ (d) $8\ \mu\text{F}$



27. Find the capacitance of the combination shown in figure (31-E16) between A and B .

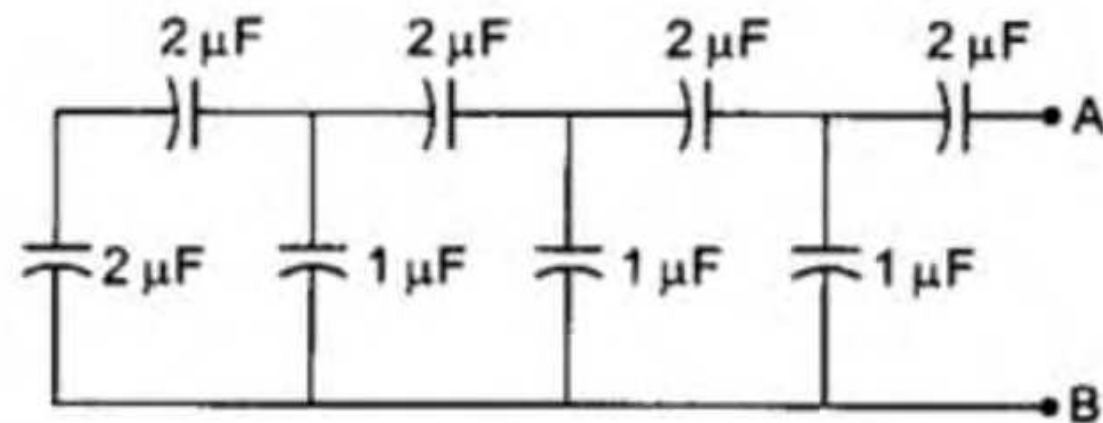


Figure 31-E16

ATDB.uno

Ans. $1 \mu\text{F}$



28. Find the equivalent capacitance of the infinite ladder shown in figure (31-E17) between the points *A* and *B*.

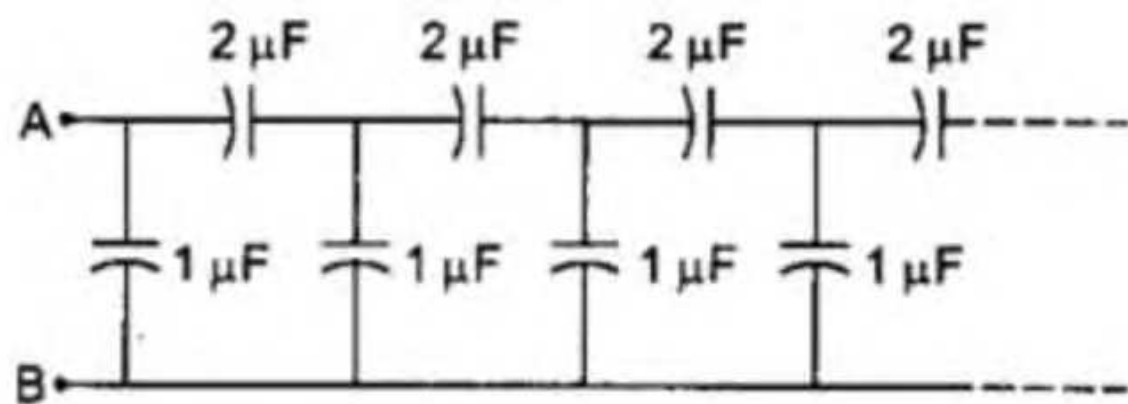


Figure 31-E17

ATDB.uno

Ans. 2 µF



32. A charge of $1\ \mu\text{C}$ is given to one plate of a parallel-plate capacitor of capacitance $0.1\ \mu\text{F}$ and a charge of $2\ \mu\text{C}$ is given to the other plate. Find the potential difference developed between the plates.

ATDB.uno

Ans. 5 V



THANK YOU

ATDB.uno